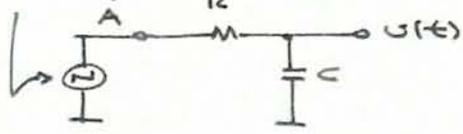


$v_{in}(t) = A \sin(\omega t)$   $u(t)$



$\frac{d(q=Cv)}{dt} \rightarrow i = C \frac{dv}{dt}$

$v(t) + RC \frac{dv(t)}{dt} = v_{in}(t)$

$v(t) \Big|_{t=0} = 0$

①  $v_h(t) = k e^{-t/RC}$

$v_h(t) + RC \frac{dv_h(t)}{dt} = 0$   
 $k e^{-t/RC} - \frac{k(RC)}{RC} e^{-t/RC} = 0 \quad (\checkmark)$

②  $v_p(t) = G e^{j\omega t}$   $\leftarrow v_p(t) + RC \frac{dv_p(t)}{dt} = e^{j\omega t}$

$G e^{j\omega t} + j\omega RC G e^{j\omega t} = e^{j\omega t}$   
 $G + j\omega RC G = 1$   
 $G = \frac{1}{1 + j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} e^{j\phi}$  ;  $\phi = -\arctan(\omega RC)$

Da mesma forma:  
 $v_p(t) + RC \frac{dv_p(t)}{dt} = e^{-j\omega t} \rightarrow v_p(t) = H e^{-j\omega t}$   
 $H e^{-j\omega t} - j\omega RC H e^{-j\omega t} = e^{-j\omega t}$   
 $H = \frac{1}{1 - j\omega RC} = \frac{1}{\sqrt{1 + (\omega RC)^2}} e^{-j\phi}$  ;  $\phi = -\arctan(\omega RC)$

Considerando entrada senoidal:

$v_{in}(t) = A (e^{j\omega t} - e^{-j\omega t})$

Saida:  $\frac{A}{\sqrt{1 + (\omega RC)^2}} \frac{(e^{j\phi} e^{j\omega t} - e^{-j\phi} e^{-j\omega t})}{2j} = v_p(t)$

$v_p(t) = \frac{A}{\sqrt{1 + (\omega RC)^2}} \sin(\omega t + \phi) = B \sin(\omega t + \phi)$

③ Solução completa (homogênea + particular):


$v(t) = k e^{-t/RC} + B \sin(\omega t + \phi)$

$t=0 \rightarrow v(0)=0 \rightarrow k + B \sin(\phi) = 0 \rightarrow k = -B \sin \phi$

Ex.:  $R = 18 \text{ k}\Omega$ ;  $C = 22 \text{ nF}$  (18 "kilo ohms", 22 "nano farads")


$f = 400 \text{ Hz}$   
 $\omega = \frac{1}{RC} = 1 \text{ rad/seg} \rightarrow 1 + \omega RC = 2 \rightarrow B = \frac{A}{\sqrt{2}}$  ;  $\phi = -45^\circ$

Alternativamente ("método dos fasores"):

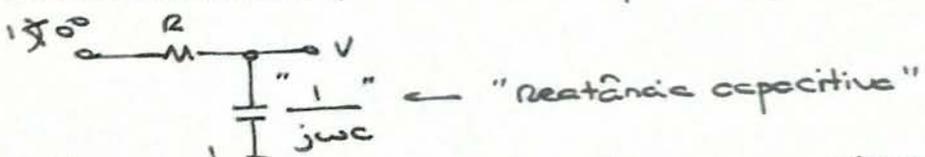

$\frac{V}{1 \angle 0^\circ} = \frac{1/j\omega C}{R + 1/j\omega C} \rightarrow v = \frac{1}{1 + j\omega RC} \rightarrow v(t) = B \sin(\omega t + \phi)$   
 $B = |V|$  ;  $\phi = \angle V$

Figuras de Lissajous:

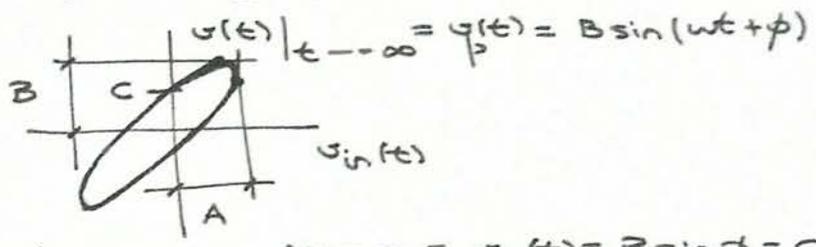



$v(t) \Big|_{t \rightarrow -\infty} = v_p(t) = B \sin(\omega t + \phi)$

"Ganho" da resposta do filtro:  $\frac{B}{A}$

$\hookrightarrow$  Em dB:  $20 \log_{10} \left( \frac{B}{A} \right)$

"fase" da resposta do filtro:  $\phi = \arcsin\left(\frac{C}{B}\right)$

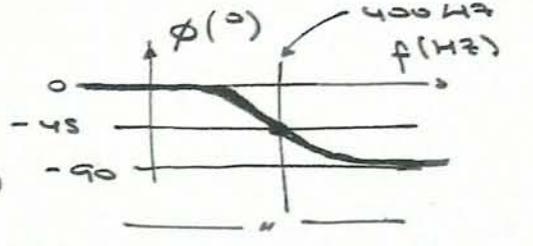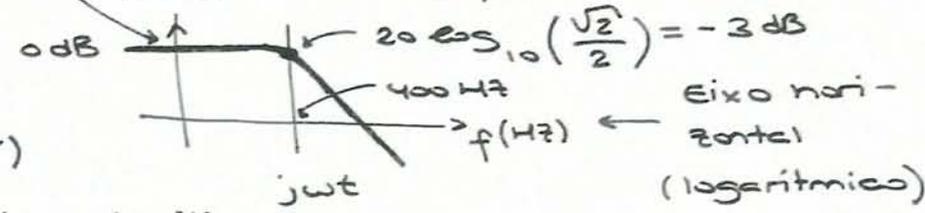$20 \log_{10} \left( \frac{B}{A} \right)$  Google: "semilog paper"



Observação:

Considere  $z = 1 + j$

Módulo de  $z$ :  $|z| = \sqrt{2}$

Fase de  $z$ :  $\arctan(1) = 45 \text{ graus}$

$1/z = 1 / (1+j) = (1-j) / 2$

Módulo de  $1/z$ :  $|1/z| = \sqrt{2}/2$

Note que o módulo de  $1/z$  é igual a  $1/|z|$

Fase de  $1/z$ :  $\arctan(-1) = -45 \text{ graus}$

Note que a fase de  $1/z$  é igual a  $- \text{fase}(z)$