

1) c) $n_i = 1.66 \times 10^{15} (300)^{3/2} \exp\left(\frac{-0.66 \times 1.6 \times 10^{-19}}{1.38 \times 10^{-23} \times 600}\right) = 1.66 \times 10^{15} \times 5.1962 \times 10^3 \times 2.89 \times 10^{-6} = 2.49 \times 10^{13} / \text{cm}^3$
($e^{-12.754} = 2.89 \times 10^{-6}$)

$n_p = n_i^2 \Rightarrow p = \frac{(2.49)^2 \times 10^{26}}{2 \times 10^{17}} \Rightarrow p = 3.1 \times 10^9 / \text{cm}^3 ; n = 2 \times 10^{17} / \text{cm}^3$

b) $E = S / (15 \times 10^{-6} \text{ m}) = S / (15 \times 10^{-4} \text{ cm}) = 10^5 \text{ V/cm}$

Material dopado: $J = 1.6 \times 10^{-19} \left(\frac{3900 \times 2 \times 10^{17}}{7.8 \times 10^{20}} + \frac{1900 \times 3.1 \times 10^9}{5.89 \times 10^{12}} \right) \times 10^5 = 1.6 \times 10^{-19} \times 7.8 \times 10^{20} \times 10^5 = 12.48 \times 10^6 \text{ A/cm}^2$

$A = 50 \times 10^{-7} (\text{cm}) \times 50 \times 10^{-7} (\text{cm}) = 2.5 \times 10^2 \times 10^{-14} = 2.5 \times 10^{-11} \text{ cm}^2$

$I = 12.48 \times 10^6 \times 2.5 \times 10^{-11} \Rightarrow I = 31.2 \times 10^{-5} \Rightarrow I = 312 \mu\text{A}$

Sem dopagem: $J = 1.6 \times 10^{-19} \left(\frac{(3900 + 1900) \times 2.49 \times 10^{13}}{1.44 \times 10^{17}} \right) \times 10^5 = 2.30 \times 10^3 \text{ A/cm}^2$

$I = 2.30 \times 10^3 \times 2.5 \times 10^{-11} \Rightarrow 5.75 \times 10^{-8} = I \Rightarrow I = 57.5 \text{ nA}$

A corrente no material dopado é $312000 / 57.5 = 5426 \text{ vezes}$ a corrente do material não dopado.

2) c) Da lado n: $N_D = 10^{17} / \text{cm}^3 = n_n$ (elétrons = portadores majoritários)
 $n_p = n_i^2 \Rightarrow p = \frac{1.664 \times 10^{20}}{10^{17}} \Rightarrow p_n = 1.664 \times 10^3 / \text{cm}^3$ (lacunas = portadores minoritários)

Da lado p: $N_A = 10^{16} / \text{cm}^3 = p_p$ (lacunas = portadores majoritários)

$n_p = n_i^2 \Rightarrow n = \frac{1.664 \times 10^{20}}{10^{16}} \Rightarrow n_p = 1.664 \times 10^4 / \text{cm}^3$ (elétrons = portadores minoritários)

b) $T = 250 \text{ K}$: $V_D = \frac{kT}{q} \ln\left(\frac{10^{16} \cdot 10^{17}}{n_i^2}\right) = 21.67 \ln(0.857 \times 10^{17}) = 21.67 \times 38.99 = 845 \text{ mV}$

$\frac{kT}{q}$: $\frac{-27.26 \text{ mV}}{250 \text{ K}} \rightarrow \frac{300 \text{ K}}{250 \text{ K}} \rightarrow \frac{26 \times 250}{300} = 21.67 \text{ mV}$
 $(11.08)^2 \times 10^{16} \leq 5.2 \times 10^{15} (250)^{3/2} \exp\left(\frac{-1.12 \times 1.6 \times 100}{1.38 \times 2 \times 2.5}\right) = n_i = 1.08 \times 10^8 / \text{cm}^3$

$T = 350 \text{ K}$: $V_D = \frac{kT}{q} \ln\left(\frac{10^{16} \cdot 10^{17}}{n_i^2}\right) = 30.33 \ln\left(\frac{10^{33}}{2.99^2 \times 10^{22}}\right) = 30.33 \ln(0.112 \times 10^{11}) = 30.33 \times 23.17 = 702 \text{ mV}$

$\frac{kT}{q}$: $\frac{26 \text{ mV}}{350 \text{ K}} \rightarrow \frac{300 \text{ K}}{350 \text{ K}} \rightarrow \frac{26 \times 350}{300} = 30.33 \text{ mV}$
 $(2.99)^2 \times 10^{22} \leq 5.2 \times 10^{15} (350)^{3/2} \exp\left(\frac{-1.12 \times 1.6 \times 100}{1.38 \times 2 \times 3.5}\right) = 2.99 \times 10^{11} / \text{cm}^3$

3) a) Começando por $I_D = \frac{0.6 - V_D}{1000} \Big|_{V_D=0.5} = 0.1 \text{ mA} = 10^{-4} \text{ A}$

temos $V_D = 26 \text{ mV} \times \ln\left(\frac{I_D}{10^{-15}}\right) = 26 \times 25.33 = 0.66 \text{ V} \rightarrow$ maior que $0.6 \text{ V} \rightarrow$ não vai convergir!

Mudando o sistema de equações, temos: $I_D = 10^{-15} \exp\left(\frac{V_D}{26 \text{ mV}}\right) \Big|_{V_D=0.5} = 225 \text{ nA}$

$V_D = 0.6 - 1000 I_D = 0.6 - 1000 \times 225 \text{ nA} = 600 \text{ mV} - 0.225 \text{ mV} = 599.8 \text{ mV}$

$I_D = 10^{-15} \exp(599.8/26) = 10442 \text{ nA} = 10.4 \mu\text{A}$

$V_D = 0.6 - 1000 \times 10.4 \times 10^{-6} = 589.6 \text{ mV}$

$I_D = 10^{-15} \exp(589.6/26) = 7054 \text{ nA} = 7.05 \mu\text{A}$

$V_D = 600 \text{ mV} - 7.1 \text{ mV} = 593 \text{ mV}$

$I_D = 10^{-15} \exp(593/26) = 8 \mu\text{A} \rightarrow V_D = 592 \text{ mV}$

$I_D = 10^{-15} \exp(592/26) = 7.7 \mu\text{A} \rightarrow V_D = 592.3 \text{ mV}$

$I_D = 7.8 \mu\text{A} \rightarrow V_D = 592.8 \text{ mV}$

b) 2.372 mA 0.623 V 0.628 V

2.372 mA 2.3 mA 1.754 mA 1.744 mA

3 V 0.7 V 1.5 mA 0.628 mA

0.27 mA 0.623 mA 0.628 mA

I: $V_D = 52 \text{ mV} \times \ln\left(\frac{1.6 \times 10^{-3}}{10^{-8}}\right) = 52 \text{ mV} \times 11.98 = 623 \text{ mV}$

II: $V_D = 52 \text{ mV} \times \ln\left(\frac{1.754 \times 10^{-3}}{10^{-8}}\right) = 52 \text{ mV} \times 12.07 = 628 \text{ mV}$


III: $V_D = 52 \text{ mV} \times \ln\left(\frac{1.744 \times 10^{-3}}{10^{-8}}\right) = 52 \text{ mV} \times 12.07 = 628 \text{ mV}$

4) a) Solução com voltagem constante (bateria):

18 mA 8.2 V $V_D = 8.2 \text{ V}$ $I_D = 9.8 \text{ mA}$

10 V 100Ω 8.2 V 8.2 mA

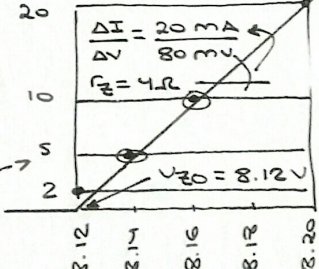Solução com modelo com bateria V_{D0} e resistência r_E :



4) Continuação:

$I_1 = I_2 + I_3$, então:

$\frac{10 - V_X}{1000} = \frac{V_X}{1000} + \frac{V_X - 8.12}{4}$

$100 - 10V_X = V_X + 250V_X - 250 \times 8.12$

$261V_X = 100 + 250 \times 8.12 \rightarrow V_X = 2130/261$

$V_X = 8.1609 \text{ V} \rightarrow I_2 = \frac{8.1609 - 8.12}{4} = 10.23 \text{ mA}$

b) Solução com voltagem constante (bateria):

220Ω 10 V 8.2 V 4.5 mA

10 V 220Ω 6Ω 0.71 V 4Ω 8.12 V I_2

$I_2 = (10 - 8.83) / 220 = 5.09 \text{ mA}$

$V_Z = 8.12 + 4 \times 5.09 \times 10^{-3} = 8.14 \text{ V}$

Solução com bateria V_{D0} e resistência r_E :

$\frac{\Delta I}{\Delta V} = \frac{20 \text{ mA}}{120 \text{ mV}}$

$r_D = 6 \Omega$

$V_{D0} = 0.71 \text{ V}$

20 10 5 2 0 0 0 0 0

5) a)

$V_P = 10.7 \text{ V}$

$P = V_{RMS}^2 / R = 10^{-3} \rightarrow R = 25 \text{ k}\Omega$

$V_{DC} = -10/\pi = -3.18 \text{ V}$

$V_{RMS} = 10/2 = 5 \text{ V}$

$V_{AC, RMS} = 3.86 \text{ V}$

b)

$V_P = 17 \text{ V}$

$V_P = 17 \text{ V}$

$V_{DC} = \frac{16.3 + 13.7}{2} = 15 \text{ V}$

$V_{AC, RMS} = \frac{1.0}{\sqrt{2}} = 0.707 \text{ V}$

$V_{RMS} = \sqrt{15^2 + 0.707^2} = 15.02 \text{ V}$

$P = V_{RMS}^2 / R = 1 \text{ mW}$

$R = 225 \text{ k}\Omega$ (o valor exato seria $225.6 \text{ k}\Omega$)