



Aluno(a):

Gabarito da Prova Parcial #2

Disciplina:

Eletrônica I — EEL315

Turma:

2018/2

Professor(a):

José Gabriel

1

2

3

4

5

Questão ①

$$a) (1 + \sqrt{3} \times 0.1) V_{DC} = 16.3 \Rightarrow V_{DC} = 13.9 \text{ V}$$

$$I_{DC} = (13.9 - 8.2) / 220 = 26 \text{ mA}$$

$$C = (26 \times 10^{-3}) / (2 \times 1.7 \times 60 \times 0.1 \times 16.3) = 0.026 / (3.4 \times 6 \times 16.3) = 0.026 / 333$$

$$C = 78 \mu\text{F} \Rightarrow \text{Usamos valor comercial } \boxed{C = 100 \mu\text{F}}$$

(Obs.: o fator de ripple será aproximadamente $26 / (3.4 \times 6 \times 16.3) = 7.8\%$)

$$b) \text{ Com } C = 220 \mu\text{F}: r = (26 \times 10^{-3}) / (2 \times 1.7 \times 60 \times 0.22 \times 10^{-3} \times 16.3) = 26 / 732 = 3.6\%$$

$$(1 + \sqrt{3} \times 0.036) V_{DC} = 16.3 \Rightarrow V_{DC} = 15.4 \text{ V}$$

$$I_{DC} = (15.4 - 8.2) / 220 = 33 \text{ mA}$$

$$\text{Segunda iteração: } r = 33 / 732 = 4.5\%$$

$$(1 + \sqrt{3} \times 0.045) V_{DC} = 16.3 \Rightarrow V_{DC} = 15.1 \text{ V} \Rightarrow I_{DC} = 31.3 \text{ mA}$$

$$\text{Terceira iteração: } r = 31.3 / 732 = 4.3\%$$



$$(1 + \sqrt{3} \times 0.043) V_{DC} = 16.3 \Rightarrow V_{DC} = 15.2 \text{ V}$$

— O diodo Zener opera com corrente máxima em torno de 33 mA ($R_L \rightarrow \infty$) e com corrente mínima em torno de 2 mA ($R_L = 270 \Omega \rightarrow I_L = 30.4 \text{ mA}$).

$$\text{Olhando a Tabela 1, temos: } V_Z = 8.117 \text{ V} \rightarrow I_Z = 2 \text{ mA}$$

$$V_Z = 8.2 \text{ V} \rightarrow I_Z = 20 \text{ mA}$$
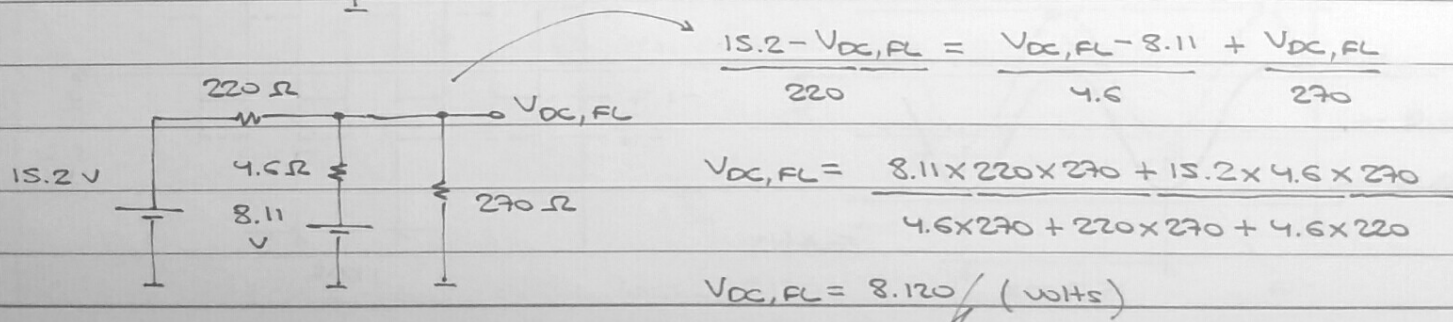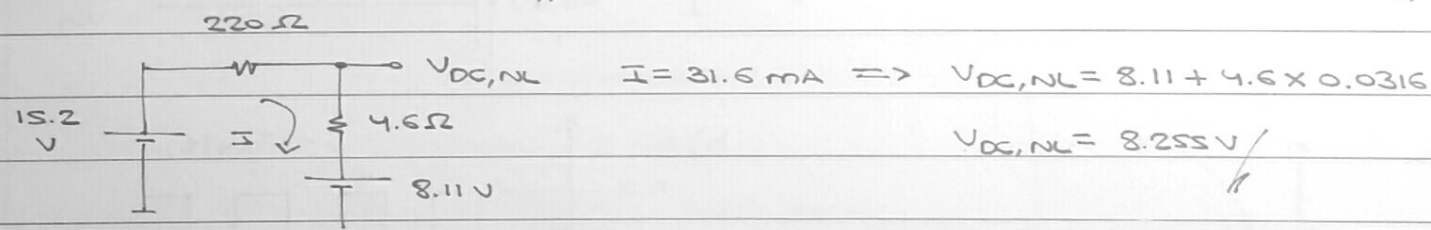
$$r_Z = \Delta V / \Delta I = 83 / 18 = 4.6 \Omega \rightarrow V_{Z0} + 4.6 \times 0.02 = 8.2 \Rightarrow V_{Z0} = 8.11 \text{ V}$$




Fator de regulac o: $(8.255 - 8.120) / 8.255 = \boxed{1.6\%}$

Quest o 2

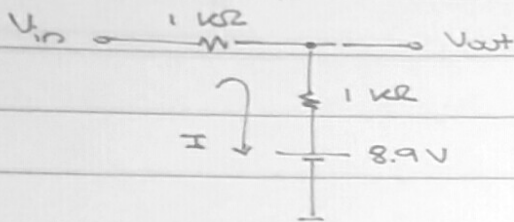a) Se $-8.9 \text{ V} < V_{in} < 8.9 \text{ V}$, os diodos est o desligados. Desprezando o resistor de $10^6 \Omega$, temos $V_{out} = V_{in}$.

Se $V_{in} > 8.9 \text{ V}$, os diodos est o ligados. Desprezando o resistor de $10^6 \Omega$:




$$I = (V_{in} - 8.9) / 2000$$

$$V_{out} = 8.9 + 1000 I = 8.9 + V_{in}/2 - 8.9/2$$

$$V_{out} = (V_{in} + 8.9) / 2$$

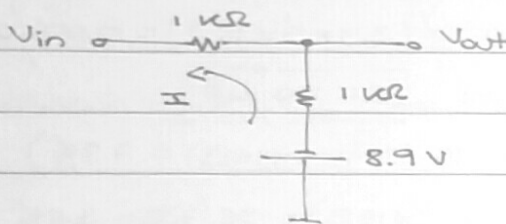
Se $V_{in} < -8.9 \text{ V}$, os diodos est o ligados. Desprezando o resistor de $10^6 \Omega$:




$$I = (-8.9 - V_{in}) / 2000$$

$$V_{out} = -8.9 - 1000 I = -8.9 + 8.9/2 + V_{in}/2$$



$$V_{out} = (V_{in} - 8.9) / 2$$

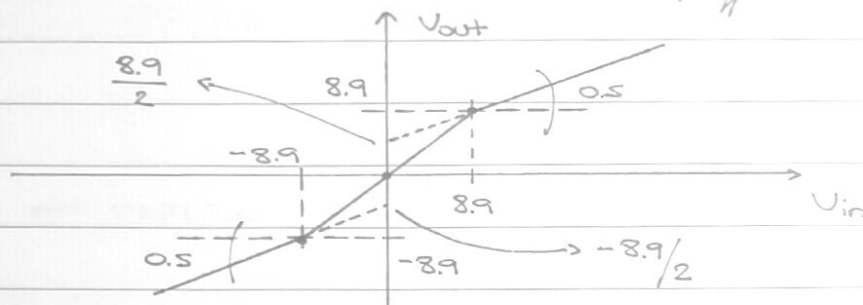

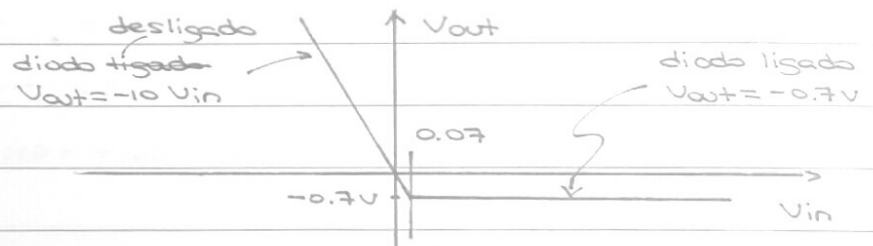b) Com o diodo desligado, temos $V_{out} = -10 V_{in}$ (configura o inversora com $R_2 = 10 R_1$). A rela o $V_{out} = -10 V_{in}$ vale desde que $V_{out} > -0.7 \text{ V}$, ou seja, desde que $V_{in} < 0.07 \text{ V}$. Quando $V_{in} > 0.07 \text{ V}$, temos o diodo ligado e $V_{out} = -0.7 \text{ V}$.




Quest o 3

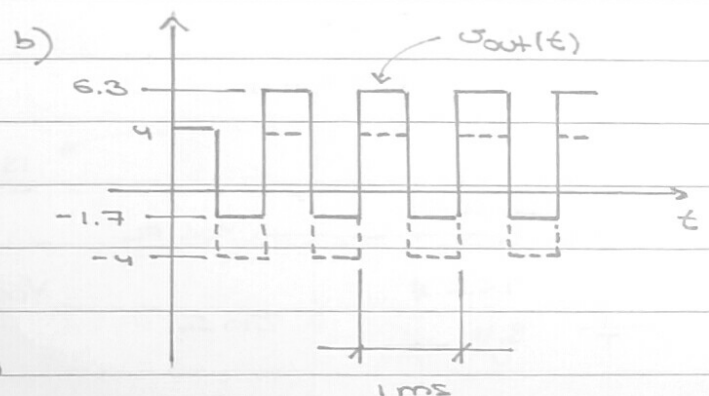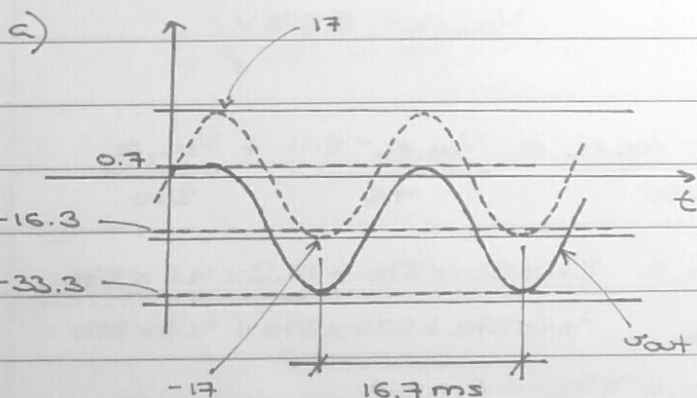


Questão (4)


a) Duas opções são:

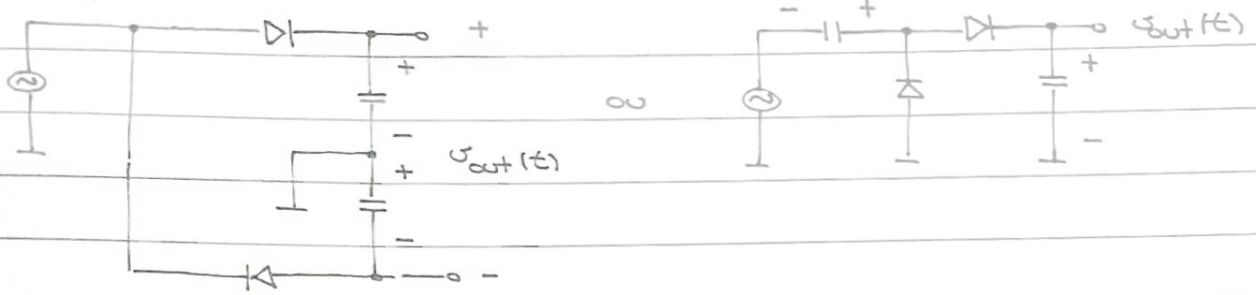

b) Duas opções são:

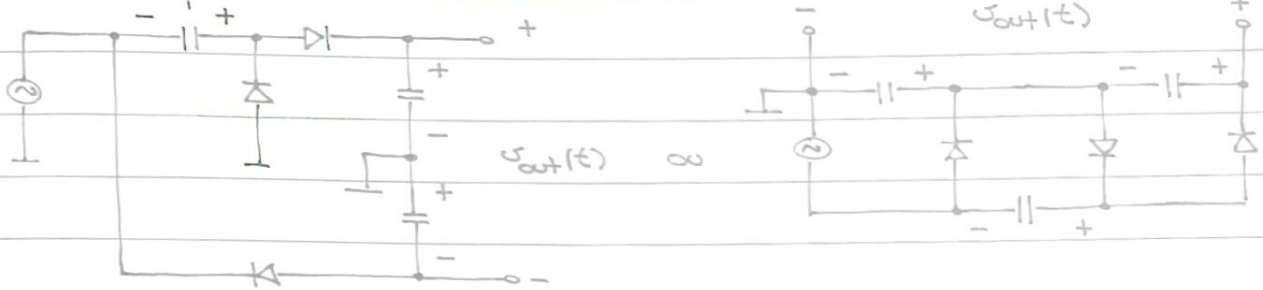

Questão (5)

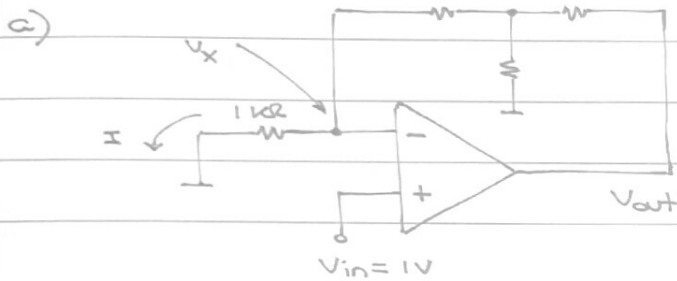


$$V_x = 1V \Rightarrow I = 1mA$$

$$V_y = V_x + 1000 \times I$$

$$V_y = 1 + \underbrace{1000 \times 1mA}_1$$
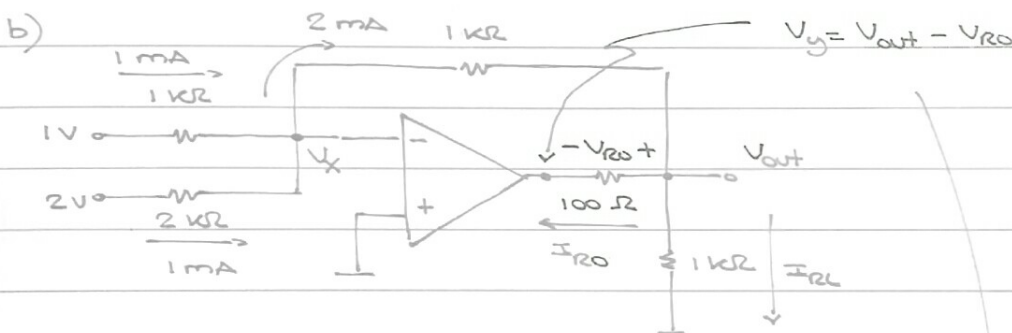
$$\boxed{V_y = 2V} \quad (\text{Obs.: } V_{out} = V_y + 1000 \times 3mA = 5V)$$



$$V_x = 0 \Rightarrow V_{out} = V_x - 1000 \times 2mA = -2V$$

$$\text{Então: } I_{R2} = -V_{out} / 1000 = -2mA$$

$$\text{Então: } I_{R0} = 2mA + 2mA \Rightarrow I_{R0} = 4mA$$

$$\text{E portanto } V_{R0} = 100 \times 4mA = 0.4V \Rightarrow V_y = -2V - 0.4V$$

$$\boxed{V_y = -2.4V}$$