



Aluno(a):

Prova Parcial #2 — Gabarito

Disciplina:

Eletrônica I

Turma:

2019/1

Professor(a):

José Gabriel

1

2

3

4

5

### Questão 1

a) Assumindo  $r = 10\%$  (chute inicial), temos  $(1 + \sqrt{3} \times 0.1) V_{DC} = 16.3$ .

$$\text{Então: } V_{DC} = 13.9 \text{ V} \rightarrow I_{DC} = (13.9 - 5.6) / 120 = 8.3 / 120 = 69 \text{ mA}$$

( $\uparrow V_Z = 5.6 \text{ V}$  quando  $I_Z \approx 20 \text{ mA}$ )

$$r = \frac{69 \times 10^{-3}}{4 \times 1.7 \times 60 \times 0.1 \times 10^{-3} \times 16.3} = \frac{69}{665.04} = \boxed{10.4\%}$$

(Recalculando:  $(1 + \sqrt{3} \times 0.104) V_{DC} = 16.3 \rightarrow V_{DC} = 13.8 \text{ V} \rightarrow I_{DC} = 68 \text{ mA}$

$$\rightarrow r = 68 / 665.05 \rightarrow r = 10.2\%$$

$(1 + \sqrt{3} \times 0.102) V_{DC} = 16.3 \rightarrow V_{DC} = 13.85 \text{ V} \rightarrow I_{DC} = 68.8 \text{ mA}$

$$\rightarrow r = 68.8 / 665.05 \rightarrow r = 10.3\%$$

Se removermos  $R_L$ , então a corrente de 69 mA é toda aplicada ao diodo



$$\text{Zener} \rightarrow \boxed{I_Z = 69 \text{ mA}}$$

(Obs.:  $V_Z = 5.4 + 10 \times 0.069 = 6.1 \text{ V} \rightarrow I_{DC} = (13.9 - 6.1) / 120 = 65 \text{ mA}$ , então


a corrente  $I_Z$  está 6% abaixo de 69 mA, por causa do aumento em

$V_Z$  (de 5.6 V para 6.1 V), mas este refinamento não é necessário).
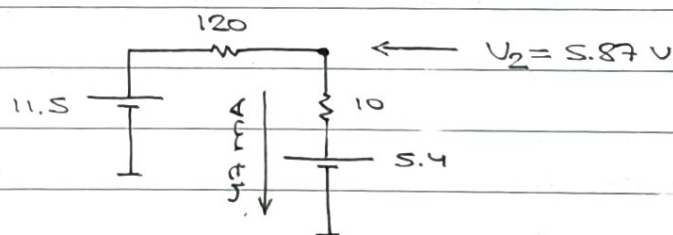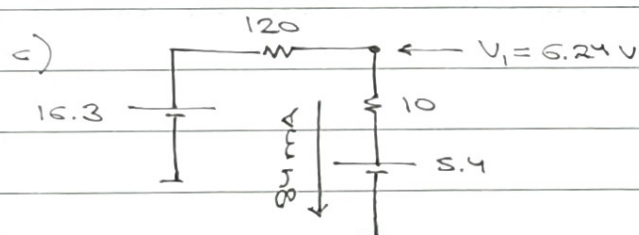
$$b) r_{RL} = 0.104 \times \frac{10}{120 + 10} \times \frac{13.9}{5.6} = 0.0199 \rightarrow \boxed{r \approx 2\%}$$



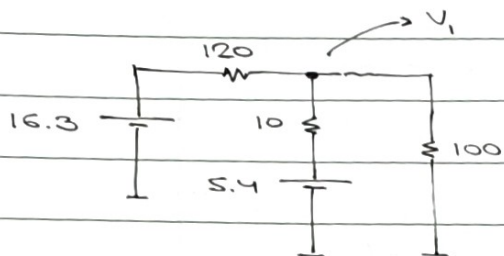
Então  $V_{OC, NL} = 6.055 \text{ V}$  (sem  $R_L$ )



$$\frac{16.3 - V_1}{120} = \frac{V_1 - 5.4}{10} + \frac{V_1}{100}$$

$$80 - 5V_1 = 60V_1 - 324 + 6V_1$$
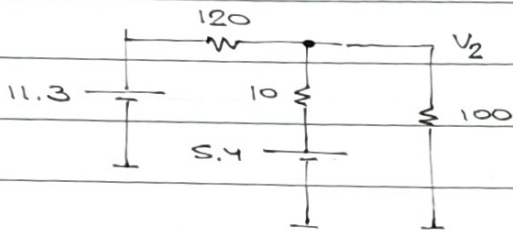
$$V_1 = (80 + 324) / 71 \rightarrow V_1 = 5.69 \text{ V}$$



$$\frac{11.3 - V_2}{120} = \frac{V_2 - 5.4}{10} + \frac{V_2}{100}$$



$$56.5 - 5V_2 = 60V_2 - 324 + 6V_2$$

$$V_2 = (56.5 + 324) / 71 \rightarrow V_2 = 5.36 \text{ V}$$



Então  $V_{OC, FL} = 5.525 \text{ V}$  ( $R_{Lmin}$ )

Fator de regulação:  $(6.055 - 5.525) / 6.055 = \boxed{8.8\%}$

Questão (2)

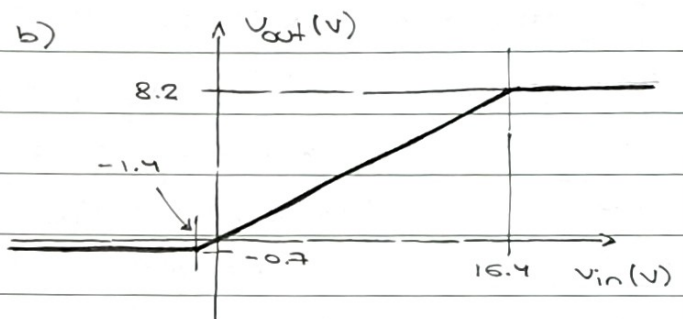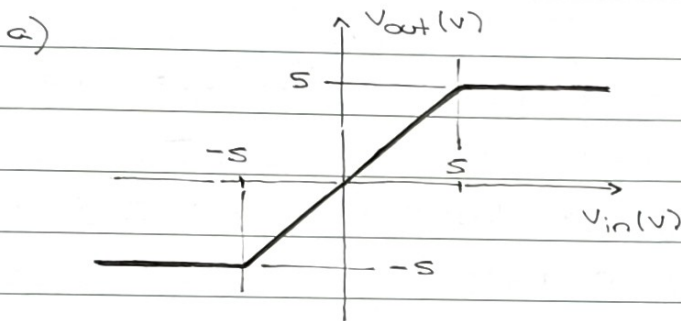

Questão (3)

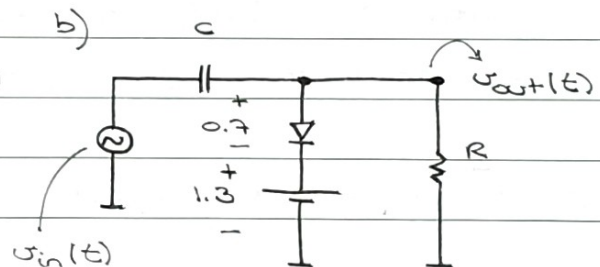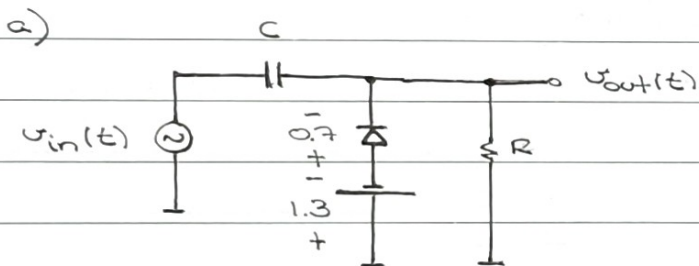

Obs.: o valor de  $C$  deve ser especificado de acordo com a frequência da onda  $v_{in}(t)$ , levando-se em conta o valor de  $R$ .

Questão (4)




a)  $\lim_{t \rightarrow \infty} v_{C2}(t) = 2 \times 10 = 20 \text{ V}$  ; b)  $\lim_{t \rightarrow \infty} v_{C3}(t) = -10 \text{ V}$

Questão (5)

a)  $V_{out} = 11 V_{in}$ , se  $|V_{out}| < 12 V$

$V_{out} = 12 V$ , se  $V_{in} > \frac{12}{11} V$

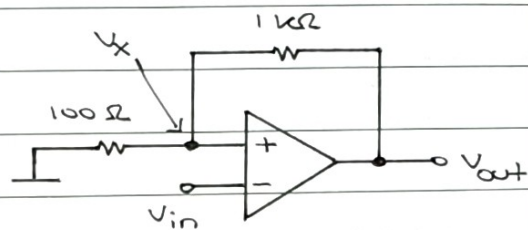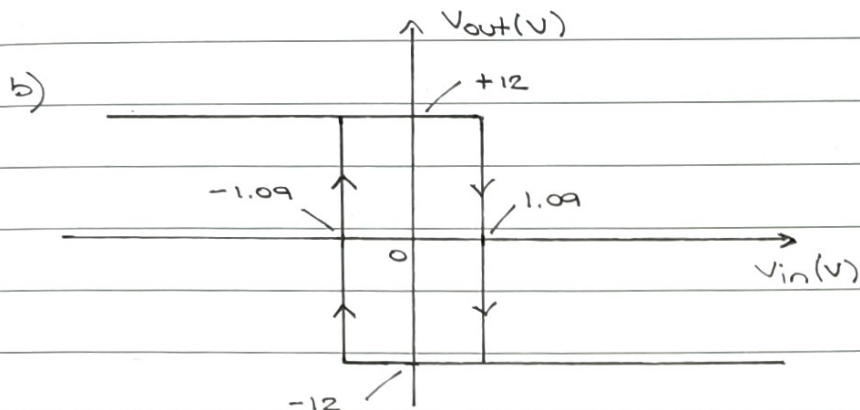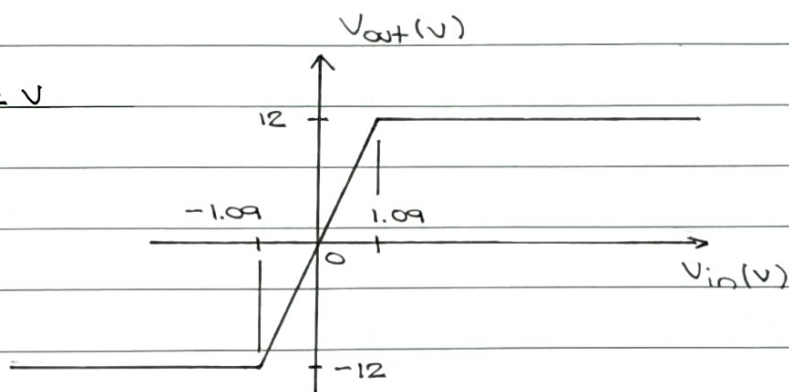$V_{out} = -12 V$ , se  $V_{in} < -\frac{12}{11} V$



Se  $V_{out} = 12 V$ , então  $V_x = \frac{12}{11} V$  ———>

$V_{out} = 12 V$ , se  $V_{in} < \frac{12}{11} V$


$V_{out} = -12 V$ , se  $V_{in} > \frac{12}{11} V$

Se  $V_{out} = -12 V$ , então  $V_x = -\frac{12}{11} V$  ———>

$V_{out} = 12 V$ , se  $V_{in} < -\frac{12}{11} V$

$V_{out} = -12 V$ , se  $V_{in} > -\frac{12}{11} V$

Item Extra:

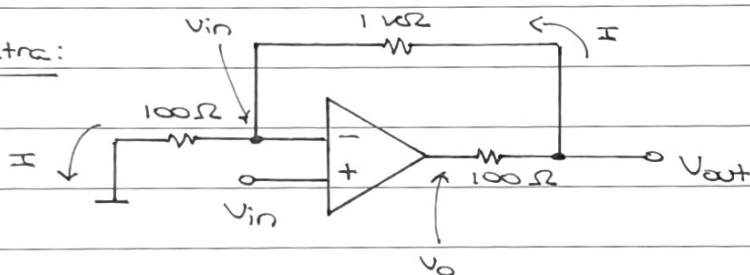

$I = \frac{V_{in}}{100} \rightarrow V_{out} = V_{in} + \frac{1000}{100} V_{in} = 11 V_{in}$

$V_0 = V_{out} + 100 I = V_{out} + V_{in} = V_{out} + \frac{V_{out}}{11} = \frac{12 V_{out}}{11}$

Por causa da clímen-

tação  $\pm 12 V$ , temos

$|V_{omax}| = 12 V$ .

Então:

$|V_{outmax}| = \frac{11}{12} |V_{omax}|$

$|V_{outmax}| = 11 V$

