



Aluno(a):

Prova Final — Gabarito

Disciplina:

Eletrônica I — EEL315

Turma:

2018/1

Professor(a):

José Gabriel

1

2

3

4

5

Questão (1)

$$N_A = 10^{16} \rightarrow p = 10^{16} / \text{cm}^3$$

$$n_p = n_i^2 \rightarrow n = (1.08 \times 10^{10})^2 / 10^{16} \rightarrow n = 1.17 \times 10^4 / \text{cm}^3$$

$$E = 5 / (0.5 \times 10^{-6}) = 10^7 \text{ V/m} = 10^5 \text{ V/cm}$$

$$J = 1.6 \times 10^{-19} (1350 \times 1.17 \times 10^4 + 480 \times 10^{16}) \times 10^5 = 480 \times 1.6 \times 10^2 = 7.68 \times 10^4 \text{ A/cm}^2$$

$$A = (50 \times 10^{-7})^2 = 2.5 \times 10^{-11} \text{ cm}^2$$

$$\text{Então } I = 7.68 \times 2.5 \times 10^{-7} \rightarrow I = 1.92 \mu\text{A}$$

Questão (2)

$$V_0 = \frac{kT}{q} \ln \left( \frac{N_A n_0}{n_i^2} \right) = \frac{26 \times 10^{-3}}{1} \ln \left( \frac{10^{16}}{1.17 \times 10^{20}} \right) = \frac{26 \times 10^{-3}}{32.08} \ln (8.547 \times 10^{13}) = 834 \text{ mV}$$

Questão (3)

Chute inicial:  $V_D = 0.6 \text{ V}$

$$\text{Então: } I_D = 10^{-15} \exp(V_D / 26 \text{ mV}) \rightarrow I_D = 10.5 \mu\text{A}$$

$$V_D = 0.5 - 2200 I_D \rightarrow V_D = 0.477 \text{ V}$$

$$I_D = 10^{-15} \exp(V_D / 0.026) \rightarrow I_D = 92.8 \text{ nA}$$

$$V_D = 0.5 - 2200 I_D \rightarrow V_D = 0.5 \text{ V}$$

$$I_D = 10^{-15} \exp(V_D / 0.026) \rightarrow I_D = 225 \text{ nA}$$

$$V_D = 0.5 - 2200 I_D \rightarrow V_D = 0.5 \text{ V} \quad (\text{exato: } 0.4995 \text{ V})$$

Questão (4)


Para corrente em torno de  $(12 - 8.2) / 1200 = 32 \text{ mA}$ , vamos usar o seguinte

modelo:  $V_{Z0} = 8.1 \text{ V}$  :  $8.1 \text{ V} \rightarrow "0 \text{ mA}"$

$8.2 \text{ V} \rightarrow 20 \text{ mA}$
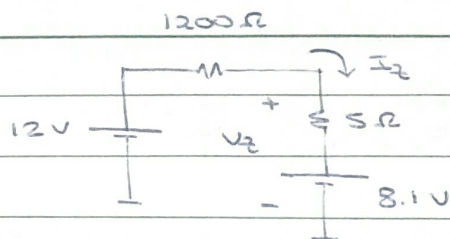
$$r_Z = \Delta V_Z / \Delta I_Z = 0.1 / 0.02 \rightarrow r_Z = 5 \Omega$$





$$I_Z = (12 - 8.1) / 1200 \rightarrow$$

$$I_Z = 3.2 \text{ mA}$$

$$V_Z = 8.1 + 5 \times 3.2 \times 10^{-3}$$

$$V_Z = 8.116 \text{ V}$$


Para corrente em torno de  $(12 - 8.2) / 180 = 21 \text{ mA}$ , vamos usar o seguinte

modelo:  $V_Z = 8.16 \text{ V} \quad I_Z = 10 \text{ mA}$

$$r_Z = \frac{\Delta V_Z}{\Delta I_Z} = \frac{0.04}{0.01} = 4 \Omega //$$

$V_Z = 8.2 \text{ V} \quad I_Z = 20 \text{ mA}$
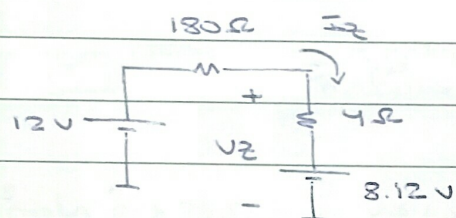
$$V_{Z0} + \underbrace{4 \times 10^{-3} \times 10}_{(10 \text{ mA})} = 8.16 \rightarrow V_{Z0} = 8.12 \text{ V} //$$



$$I_Z = (12 - 8.12) / 180 \rightarrow$$


$$I_Z = 21.1 \text{ mA}$$

$$V_Z = 8.12 + 4 \times 21.1 \times 10^{-3}$$

$$V_Z = 8.204 \text{ V}$$

Obs.: se usássemos o modelo anterior ( $V_{Z0} = 8.1 \text{ V}$  e  $r_Z = 5 \Omega$ ), encontraríamos  $I_Z = 21.1 \text{ mA}$  e  $V_Z = 8.205 \text{ V}$  (ou também — erros inferiores a 0.05% em relação ao modelo  $V_{Z0} = 8.12 \text{ V}$  e  $r_Z = 4 \Omega$ ).

Questão 5

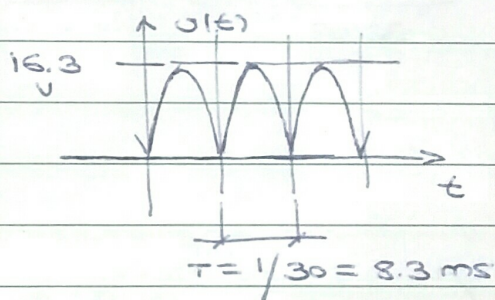

$$V_{DC} = 2 \times 16.3 / \pi = 10.38 \text{ V}$$

$$V_{RMS} = 16.3 / \sqrt{2} = 11.53 \text{ V}$$

$$V_{AC, RMS} = \sqrt{11.53^2 - 10.38^2} = 5.02 \text{ V}$$

$$r = 5.02 / 10.38 \rightarrow r = 48\%$$

$$P = \frac{11.53^2}{120} \rightarrow P = 1.11 \text{ W}$$

Questão 6

Chute inicial:  $r = 0.05 \rightarrow V_{DC} = 16.3 / (1 + \sqrt{3} \times 0.05) \rightarrow V_{DC} = 15 \text{ V}$

$$I_{DC} = 15 / 120 = 125 \text{ mA}$$

Repetindo:  $r = 125 \times 10^{-3} / (4 \times 1.7 \times 60 \times 0.47 \times 10^{-3} \times 16.3) = 125 / 3126 = 4\%$

$$V_{DC} = 16.3 / (1 + \sqrt{3} \times 0.04) \rightarrow V_{DC} = 15.3 \text{ V}$$

$$I_{DC} = 15.3 / 120 = 128 \text{ mA}$$

$$r = 128 / 3126 \rightarrow r = 4.1\%$$



### Questão 7

Chute inicial:  $V_{oc} = 15V \rightarrow I_{oc} = (15 - 8.2) / 120 = 57 \text{ mA}$

$$r = 57 \times 10^{-3} / (4 \times 1.7 \times 60 \times 0.47 \times 10^{-3} \times 16.3) = 57 / 3126 = 1.8\%$$

Repetindo:  $V_{oc} = 16.3 / (1 + \sqrt{3} \times 0.018) \rightarrow V_{oc} = 15.8V$

$$I_{oc} = (15.8 - 8.2) / 120 = 63 \text{ mA}$$


$$r = 63 / 3126 \rightarrow \boxed{r = 2\%}$$

Fator de ripple e  
voltage DC no capacitor.


Modelo do diodo Zener: vamos assumir  $V_Z \approx 8.2V$  (correntes em torno de 20 mA) e  $r_Z \approx 5\Omega$  (da Questão 4).

$$r_L = 0.02 \times \frac{5}{125} \times \frac{15.8}{8.2} \rightarrow \boxed{r_L = 0.15\%}$$


### Questão 8

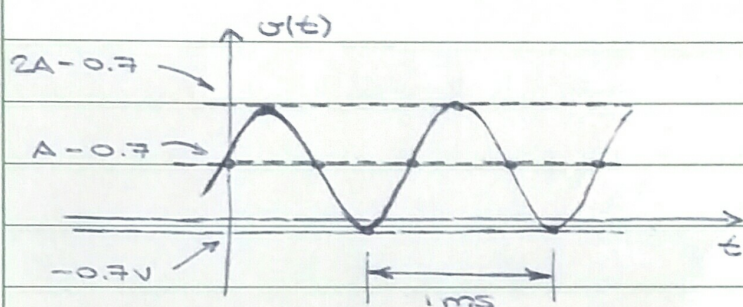

### Questão 9

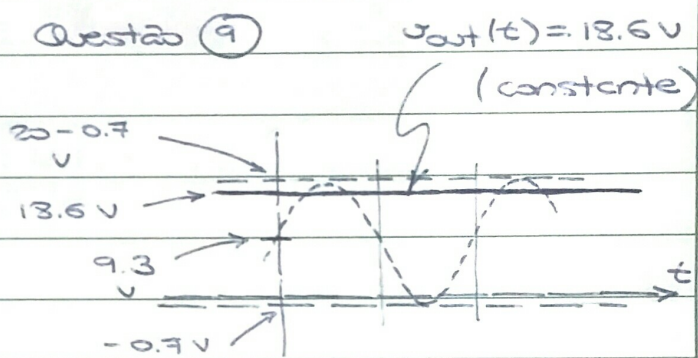

### Questão 10

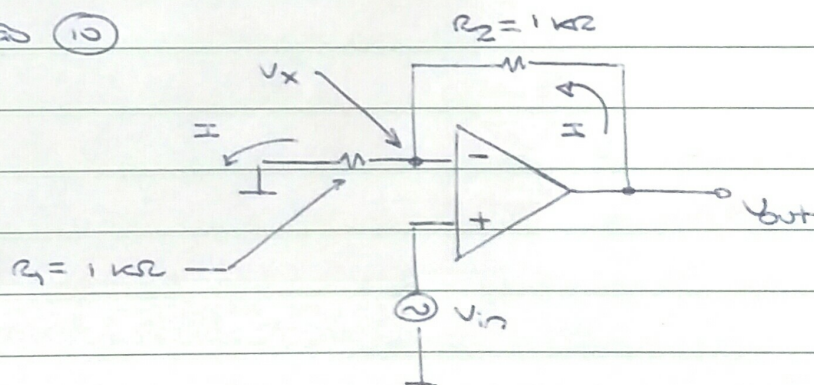

$$1000(V_{in} - V_x) = V_{out}$$

Então:

$$V_x = V_{in} - \frac{V_{out}}{1000}$$

$$I = \left( V_{in} - \frac{V_{out}}{1000} \right) / R_1$$

$$V_{out} = \left( V_{in} - \frac{V_{out}}{1000} \right) + R_2 \left( V_{in} - \frac{V_{out}}{1000} \right) / R_1 = 2V_{in} - \frac{2V_{out}}{1000}$$

$$V_{out} \left( 1 + \frac{2}{1000} \right) = 2V_{in} \rightarrow \frac{V_{out}}{V_{in}} = \frac{2}{1.002} \rightarrow \boxed{\frac{V_{out}}{V_{in}} = 1.996}$$

"vírgula"