



Aluno(a):

Prova Parcial #1 — Gabarito

Disciplina:

Eletrônica I

Turma:

2018/2

Professor(a):

José Gabriel

① a) $n = 2 \times 10^{16} \text{ elétrons/cm}^3$ ($= N_D$)

$$n_i^2 = 1.1664 \times 10^{20} / \text{cm}^6 \rightarrow p = n_i^2 / n \rightarrow p = 5.832 \times 10^3 \text{ lacunas/cm}^3$$

b) $E = 10 / (2 \times 10^{-4} \text{ cm}) = 5 \times 10^4 \text{ V/cm}$

$$J = 1.6 \times 10^{-19} \times (1350 \times 2 \times 10^{16}) \times 5 \times 10^4 = 1.6 \times 1.35 \times 2 \times 5 \times 10^4 = 2.16 \times 10^5 \text{ A/cm}^2$$

(note que $\mu_{nn} \gg \mu_{pp}$)

$$A = (100 \times 10^{-7} \text{ cm}) \times (100 \times 10^{-7} \text{ cm}) = 10^{-10} \text{ cm}^2$$

$$I = 2.16 \times 10^{-5} \text{ A} \rightarrow I = 21.6 \mu\text{A}$$

② a) $n_i = 1.66 \times 10^{15} \times 350^{1.5} \exp\left(\frac{-0.66 \times 1.6 \times 10^{-19}}{2 \times 1.38 \times 10^{-23} \times 350}\right) = 1.66 \times 6.548 \times 10^{18} \times 1.79 \times 10^{-5}$

$$\exp\left(\frac{-0.66 \times 1.6 \times 100}{2 \times 1.38 \times 3.5}\right) = \exp(-10.93) = 1.79 \times 10^{-5}$$

$$\text{Então: } n_i = 1.946 \times 10^{14} / \text{cm}^3$$

$$kT/q = 1.38 \times 10^{-23} \times 350 / (1.6 \times 10^{-19}) = 30.19 \text{ mV}$$

$$V_0 = 30.19 \times 10^{-3} \times \ln\left(\frac{2 \times 10^{34}}{3.787 \times 10^{28}}\right) = 30.19 \times 10^{-3} \times \ln(5.281 \times 10^5) \Rightarrow V_0 = 398 \text{ mV}$$

b) $\frac{N_{AND}}{N_A + N_D} = \frac{2 \times 10^{34}}{3 \times 10^{17}} = 6.67 \times 10^{16}$ (usando E_{Si} mesmo, em vez de E_{Ge}) (*)

$$C_{jo}^2 = \frac{11.7 \times 8.85 \times 10^{-14} \times 1.6 \times 10^{-19} \times 6.67 \times 10^{16} \times 1}{2 \times 0.398 \times 0.796} = \frac{1105.03 \times 10^{-17}}{0.796} = 138.82 \times 10^{-16}$$

$$C_{jo} = 11.78 \times 10^{-8} \text{ F/cm}^2$$

$$C_j = \frac{11.78}{\sqrt{1 + \frac{2}{0.398}}} = \frac{11.78}{2.455} = 4.8 \times 10^{-8} \text{ F/cm}^2$$

(*) Usando

$$E_{Ge} = 16 \times 8.85 \times 10^{-14} \text{ F/cm}, \text{ temos:}$$

$$C_{jo}^2 = 189.84 \times 10^{-16} \text{ F}^2/\text{cm}^4$$

$$C_{jo} = 13.78 \times 10^{-8} \text{ F/cm}^2$$


$$C_j = 5.6 \times 10^{-8} \text{ F/cm}^2$$

$$C = 0.56 \text{ fF}$$

$$1 \mu\text{m}^2 = 10^{-8} \text{ cm}^2$$

$$C = 4.8 \times 10^{-16} \text{ F} \rightarrow C = 0.48 \text{ fF}$$

③ a)

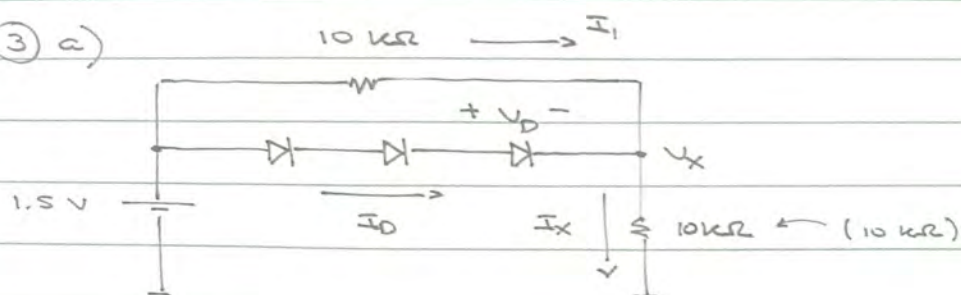

$$\frac{1.5 - V_X}{10^4} + I_D = \frac{V_X}{10^4} \quad \Rightarrow \quad V_X = 1.5 - 3V_D$$

$$1.5 - V_X + 10^4 I_D = V_X$$

$$10^4 I_D = 2V_X - 1.5 \quad \rightarrow \quad 10^4 I_D = 3 - 6V_D - 1.5 \quad \rightarrow \quad V_D = \frac{1.5 - 10^4 I_D}{6}$$

Chute inicial: $V_D = 0.25 \text{ V}$

$$1) I_D = 10^{-8} \exp(0.25/0.052) = 1.22 \mu\text{A}$$

$$V_D = (1.5 - 1.22 \times 10^{-2})/6 = 0.248 \text{ V}$$

$$2) I_D = 10^{-8} \exp(0.248/0.052) = 1.18 \times 10^{-8} = 1.18 \mu\text{A}$$

$$V_D = (1.5 - 1.18 \times 10^{-2})/6 = 0.248 \text{ V} \quad \rightarrow \quad \boxed{V_D = 0.248 \text{ V}} \quad \text{e} \quad \boxed{I_D = 1.18 \mu\text{A}}$$

Obs.: com chute inicial $V_D = 0.5 \text{ V}$, teríamos:

$$I_D = 10^{-8} \exp(0.5/0.052) = 15 \times 10^{-5} = 150 \mu\text{A}$$

$$V_D = (1.5 - 0.15)/6 = 0.225 \dots \text{ e assim por diante (converge corretamente)}$$

b) Chute inicial: $V_D = 0.7 \text{ V}$ (usamos o mesmo diagrama do item (a), com 20 V)

$$1) V_X = 20 - 3V_D \Rightarrow V_X = 17.9 \text{ V}$$

$$I_X = 1.79 \text{ mA}$$

$$I_1 = (20 - 17.9)/10 \text{ k}\Omega = 0.21 \text{ mA}$$

$$I_D = I_X - I_1 = 1.58 \text{ mA}$$

$$V_D = (52 \text{ mV}) \times \ln(1.58 \times 10^{-3}/10^{-8})$$

$$V_D = (52 \text{ mV}) \times 11.97 = 622 \text{ mV}$$

$$2) V_X = 20 - 3V_D \Rightarrow V_X = 18.13 \text{ V}$$

$$I_X = 1.81 \text{ mA}$$

$$I_1 = 1.866/10 \text{ k}\Omega = 0.19 \text{ mA}$$

$$I_D = I_X - I_1 = 1.62 \text{ mA}$$


$$V_D = (52 \text{ mV}) \times \ln(1.62 \times 10^{-3}/10^{-8})$$

$$V_D = (52 \text{ mV}) \times 12 = 624 \text{ mV}$$

3) $V_X = 20 - 3V_D \Rightarrow V_X = 18.13 \text{ V}$ (mesmo V_X da iteração 2)

$$\text{Então: } \boxed{V_D = 0.624 \text{ V}} \quad \text{e} \quad \boxed{I_D = 1.62 \text{ mA}}$$

④ a)

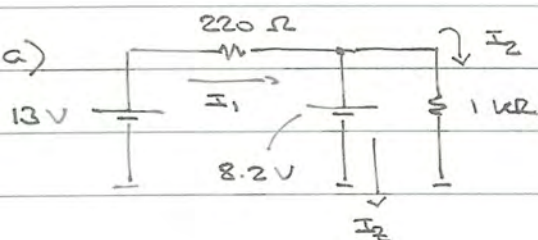

$$I_1 = (13 - 8.2)/220 = 21.8 \text{ mA}$$

$$I_2 = 8.2/1000 = 8.2 \text{ mA}$$

$$I_D = I_1 - I_2 \Rightarrow \boxed{I_D = 13.6 \text{ mA}}$$

$$\boxed{V_D = 8.2 \text{ V}}$$

Para corrente em torno de 13.6 mA, vamos


(modelo bateria)

usar o seguinte modelo: 8.16 V — 10 mA

(com V_{DO} e r_D) 8.2 V — 20 mA

$$r_z = \Delta V_z / \Delta I_z = 0.04 / 0.01 \rightarrow r_z = 4 \Omega //$$
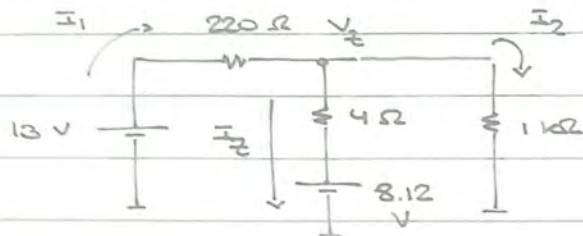
$$V_{z0} + r_z I_z = V_z \rightarrow V_{z0} + 4 \times 0.02 = 8.2 \rightarrow V_{z0} = 8.12 \text{ V} //$$



$$I_2 + I_z = I_1$$

$$\frac{V_z}{1000} + \frac{V_z - 8.12}{4} = \frac{13 - V_z}{220}$$

$$V_z (4 \times 220 + 220 \times 1000 + 4 \times 1000) = 13 \times 4 \times 1000 + 8.12 \times 220 \times 1000$$

$$V_z = 1838400 / 224880 \rightarrow \boxed{V_z = 8.175 \text{ V}} \text{ e } \boxed{I_z = 13.8 \text{ mA}}$$



$$I_1 = (13 - 2.1) / 680 = 16 \text{ mA}$$

$$I_2 = 2.1 / 1000 = 2.1 \text{ mA}$$

$$I_D = I_2 - I_1 \Rightarrow \boxed{I_D = 13.9 \text{ mA}}$$

$$\boxed{V_D = 0.7 \text{ V}}$$

Para corrente em torno de 13.9 mA, vamos usar

(modelo bateria)

O seguinte modelo (V_{D0}, r_D): 0.692 V — 10 mA

0.727 V — 20 mA

$$r_D = \Delta V_D / \Delta I_D = 0.035 / 0.01 \rightarrow r_D = 3.5 \Omega //$$

$$V_{D0} + r_D I_D = V_D \rightarrow V_{D0} + 3.5 \times 0.02 = 0.727 \rightarrow V_{D0} = 0.657 \text{ V} //$$



$$I_2 + I_D = I_1$$

$$\frac{V_X}{1000} + \frac{V_X - 1.971}{10.5} = \frac{13 - V_X}{680}$$

$$V_X (10.5 \times 680 + 1000 \times 680 + 1000 \times 10.5) = 13 \times 10.5 \times 1000 + 1.971 \times 680 \times 1000$$

$$V_X = 1476780 / 697640 = 2.117 \rightarrow \boxed{V_D = 0.706 \text{ V}} \text{ e } \boxed{I_D = 14 \text{ mA}}$$

$$\textcircled{5} \text{ a) } (1 + \sqrt{3} \times 0.04) V_{DC} = 9.3 \rightarrow V_{DC} = 8.7 \text{ V}$$

$$I_{DC} = 8.7 / 470 \rightarrow I_{DC} = 18.5 \text{ mA}$$

$$C = \frac{I_{DC}}{2\sqrt{3} f r V_m} = \frac{18.5 \times 10^{-3}}{2 \times 1.7 \times 60 \times 0.04 \times 9.3} = 244 \mu\text{F} \Rightarrow \boxed{C = 330 \mu\text{F}}$$

(meia onda) \rightarrow (valor comercial)

$$\text{b) } r = 18.5 \times 10^{-3} / (2 \times 1.7 \times 60 \times 9.3 \times 330 \times 10^{-6}) = 3\%$$

$$(1 + \sqrt{3} \times 0.03) V_{DC} = 9.3 \rightarrow V_{DC} = 8.84 \text{ V} \rightarrow I_{DC} = \frac{8.84}{470} = 18.8 \text{ mA}$$

$$r = 18.8 \times 10^{-3} / (2 \times 1.7 \times 60 \times 9.3 \times 330 \times 10^{-6}) \Rightarrow r = 3\% \text{ (} V_{eL}(t) \text{)}$$

Com relação a $v_{IN}(t)$: $V_{DC} = 0 \text{ V}$; $V_{AC,RMS} = V_{RMS} = V_p/\sqrt{2} = 7.1 \text{ V}$

$$r = V_{AC,RMS} / V_{DC}, \text{ então } r \rightarrow \infty$$

Com relação a $v_{RL}(t)$: $V_{DC} = 8.84 \text{ V}$; $r = 3\%$

$$V_{AC,RMS} = r \cdot V_{DC} \rightarrow V_{AC,RMS} = 0.265 \text{ V}$$

$$V_{RMS} = \sqrt{V_{DC}^2 + V_{AC,RMS}^2} \rightarrow V_{RMS} = 8.84 \text{ V}$$

$$P = \frac{V_{RMS}^2}{R_L} = \frac{8.84^2}{470} \rightarrow P = 166 \text{ mW}$$

— " —