



Aluno:

Gabriel da Prova Parcial #2

Disciplina:

Eletrônica I

Turma:


2019-2

Professor:

José Gabriel

1	
2	
3	
4	
5	

Questão ①

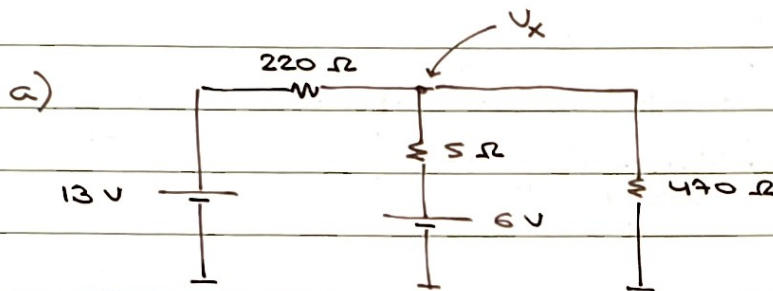

$$\frac{13 - V_x}{220} = \frac{V_x - 6}{5} + \frac{V_x}{470}$$

$$V_x (220 \times 470 + 220 \times 5 + 5 \times 470) =$$

$$13 \times 5 \times 470 + 6 \times 220 \times 470$$

$$V_x = 650950 / 106850 = 6.09 \text{ V}$$

Para 17V: $V_x = ((17) \times 5 \times 470 + 6 \times 220 \times 470) / 106850 = 660350 / 106850 = 6.18 \text{ V}$

(Obs.: fator de ripple $r_{RL} = (6.18 - 6.09) / (2\sqrt{3} \times 6.135) = 0.42\%$)

b) No capacitor: $r_{cap} = (17 - 13) / (2\sqrt{3} \times 15) = 7.7\%$

No resistor de carga: $r_{RL} = 0.077 \times (5/225) \times 15/6.2 = 0.41\%$

(assumindo que o diodo Zener é de 6.2V, ou seja, $V_Z = 6.2 \text{ V}$)



c) Quando $R_L = 220 \Omega$ e $V_{\text{capacitor}} = 13 \text{ V}$, temos $(13 - V_x)/220 = (V_x - 6)/5 + V_x/220$,
ou seja, $(220 + 10)V_x = 13 \times 5 + 6 \times 220$, então $V_x = 6.02 \text{ V}$ e portanto

$$I_{Z\min} = (6.02 - 6)/5 = 4 \text{ mA}$$



Quando $R_L \rightarrow \infty$ e $V_{\text{capacitor}} = 17 \text{ V}$, temos $I_{Z\max} = (17 - 6)/225 = 49 \text{ mA}$

(obs.: $V_x = 6 + 5 \times 0.049 = 6.25 \text{ V}$)

Questão ②

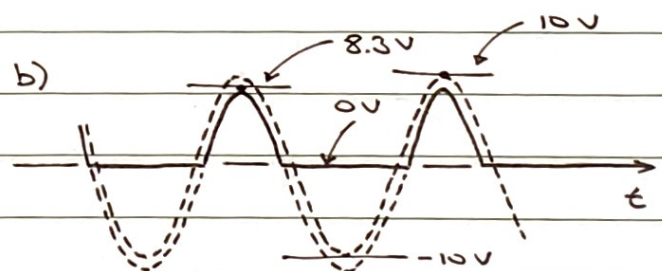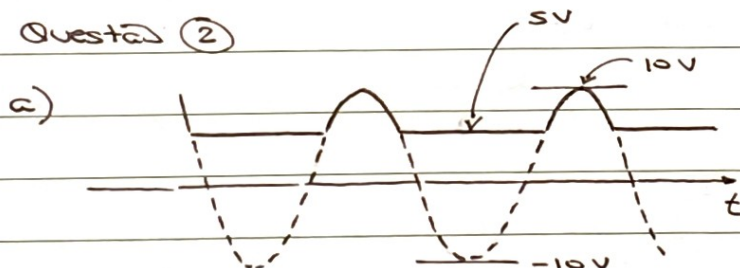

Questão ③

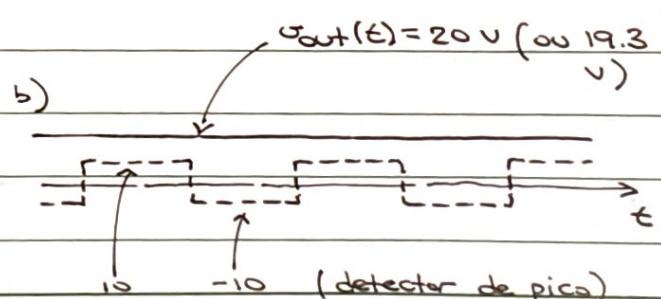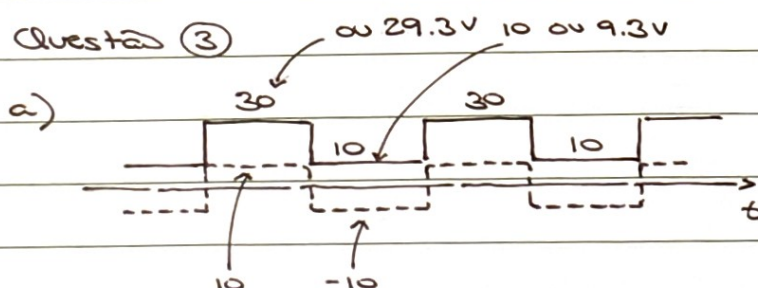

Questão (4)

$$V_{out} = 20 \text{ V} - 2 \times 1.4 \text{ V} \Rightarrow V_{out} = 18.6 \text{ V/h}$$

Questão (5)

a) $V_+ = V_2/2 = 2 \text{ V}$

$A \rightarrow \infty$, então $V_- = 2 \text{ V}$

$$V_{out} = V_- + \underbrace{(V_- - V_1)}_{0 \text{ V}} \rightarrow V_{out} = 2 \text{ V/h}$$

b) $V_+ = V_2/2 = 2 \text{ V}$

$A = 100$, então $V_{out} = 100 (V_+ - V_-)$

$$2 - V_- = V_{out}/100 \rightarrow V_- = 2 - V_{out}/100$$

$$V_{out} = V_- + (V_- - V_1) = 2 - \frac{V_{out}}{100} + \cancel{2} - \frac{V_{out}}{100} - \cancel{2}$$

$$V_{out} (1 + \frac{2}{100}) = 2$$

$$V_{out} = 2/1.02 = 1.96 \text{ V/h}$$

— " — " —