



Aluno:

Prova Final — Gabarito

Disciplina:

Eletônica I

Turma:

2019/1

Professor:

José Gabriel

1

2

3

4

5

Questão (1)

$$(dn/dx) = -2 \times 10^{17} / (5 \times 10^{-4}) = -4 \times 10^{20} \text{ cm}^{-4}; (dp/dx) = 5 \times 10^{16} / (5 \times 10^{-4}) = 10^{20} \text{ cm}^{-4}$$

$$J = 1.6 \times 10^{-19} \times (-34 \times 4 \times 10^{20} - 12 \times 10^{20}) = -2368 \text{ A/cm}^2$$

$$I = J.A = -2368 \times 200 \times 10^{-7} \times 200 \times 10^{-7} = -2368 = 9.47 \times 10^{-7} = 0.95 \text{ mA}$$

Questão (2)

$$0.026 \times \ln(N_{AND} / (1.08^2 \times 10^{20})) = 0.7 \rightarrow N_{AND} = 1.1664 \times 10^{20} \exp(26.9231) = 5.7465 \times 10^{31}$$

$$T = 400 \text{ K} \rightarrow (kT/q) = 0.026 \times (4/3) = 0.0347 \text{ V}$$

$$n_i = \frac{5.2 \times 10^{15} \times 400^{1.5} \times \exp(-1.12 \times 1.6 \times 10^{-19} / (2 \times 1.38 \times 10^{-23} \times 400))}{(4.16 \times 10^{-19}) (8.925 \times 10^{-8})} = 3.713 \times 10^{12}$$

$$V_b = 0.0347 \times \ln \left(\frac{5.7465 \times 10^{31}}{(3.713^2 \times 10^{24})} \right) = 0.529 \text{ V}$$

Questão (3)

"Chute" inicial: $V_i = 0.8 \text{ V}$ ($V_D = 0.7 \text{ V}$)

Atualizando correntes: $I_1 = 0.8 \text{ mA}$ e $I_2 = 0.7 \text{ mA}$,

então $I_D = 0.1 \text{ mA}$.

$$\text{Recalculando } V_D: V_D = 1.98 \times 0.026 \times \ln(0.1 \times 10^{-3} / (14.1 \times 10^{-9})) = 0.4565 \text{ V}$$

Mais algumas iterações

$I_1(\text{mA})$ $I_2(\text{mA})$ $I_D(\text{mA})$ $V_D(\text{V})$


1.0435 0.4565 0.5870 → 0.5476

0.9524 0.5476 0.4048 → 0.5284

0.9716 0.5284 0.4432 → 0.5331

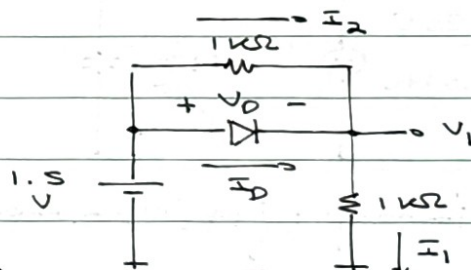0.9669 0.5331 0.4338 → 0.5320

$V_i = 0.968 \text{ V}$ ← 0.9680 0.5320 0.4360 → 0.5323 ✓



Questão (4)

DSN756

DSN4003

Modelos de bateria: $V_0 = 8.2V + 0.7V = 8.9V$ (obs.: $I = 11mA$)

Modelos lineares por partes:

DSN4003: $0.692V$ — $10mA$ $\Delta V/\Delta I = 35/10 = 3.5\Omega$ $0.657V$

$0.727V$ — $20mA$ $(\Delta V/\Delta I)$ $V_{20} = 0.727 - 3.5 \times 0.02 = \checkmark$

DSN756: $8.161V$ — $10mA$ $\Delta V/\Delta I = 39/10 = 3.9\Omega = r_2$

$8.2V$ — $20mA$ $V_{20} = 8.2 - 3.9 \times 0.02 = 8.122V$

$I = (10 - 8.122 - 0.657) / (100 + 3.5 + 3.9) = 1.221 / 107.4 = 11.4mA$

$V_0 = 8.122 + 0.657 + (3.5 + 3.9) \times 0.0114 \rightarrow V_0 = 8.863V$

Questão (5)


$V_{DC} = 2V$

$$V_{AC,RMS}^2 = \frac{1}{T} \left(\int_0^{T/2} 2^2 dt + \int_{T/2}^T (-2)^2 dt \right) = 4 \rightarrow V_{AC,RMS} = 2V$$

$$V_{RMS} = \sqrt{V_{DC}^2 + V_{AC,RMS}^2} = \sqrt{4 + 4} = \sqrt{8}$$

$$P = V_{RMS}^2 / 100 = 8 / 100 = 80mW$$

Questão (6)

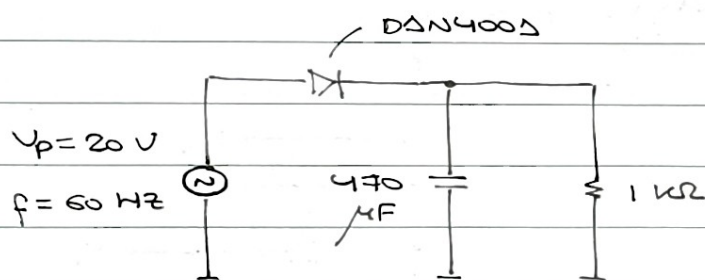

"Chute" inicial: $r = 0.1$

$$(1 + \sqrt{3} \times 0.1) V_{DC} = 19.3$$

$$V_{DC} = 16.5V$$

$$I_{DC} = V_{DC} / (1k\Omega) = 16.5mA$$

$$2\sqrt{3} \times 60 \times 0.47 \times 10^{-3} \times 19.3 = 1.885$$

$$r = 0.0165 / 1.885 = 0.0088$$

$$2^{\text{a}} \text{ iteração: } (1 + \sqrt{3} \times 0.0088) V_{DC} = 19.3 \rightarrow V_{DC} = 19.0V$$

$$I_{DC} = 19mA \rightarrow r = 0.019 / 1.885 = 0.0101 \rightarrow r = 1.01\%$$


$$3^{\text{a}} \text{ iteração: } (1 + \sqrt{3} \times 0.0101) V_{DC} = 19.3 \rightarrow V_{DC} = 19.0V$$

Questão (7)

$$r = 0.1 : (1 + \sqrt{3} \times 0.1) V_{DC} = 16.3$$

$$V_{DC} = 13.9V$$
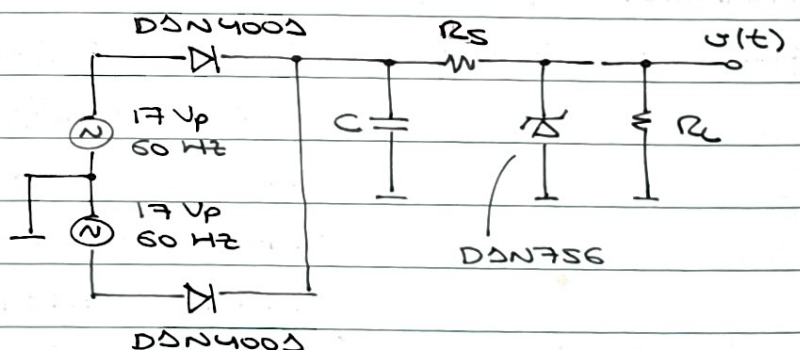
$$V_1 = 16.3V ; V_{DC} = 13.9V ; V_2 = 11.5V$$



$$(16.3 - 8.2) / R_{Smin} = 0.070 \rightarrow R_{Smin} = 115 \Omega$$

$$(11.5 - 8.2) / R_{Smax} = \underbrace{(8.2 / 470)}_{(17.4 \text{ mA})} + \underbrace{5 \text{ mA}}_{\text{"I}_{zmin}\text{"}, \text{ escolhida arbitrariamente}} \rightarrow R_{Smax} = 147 \Omega$$

$$115 \Omega < R_S < 147 \Omega \rightarrow R_S = 120 \Omega //$$

$$I_{DC} = (13.9 - 8.2) / 120 = 47.5 \text{ mA}$$

$$C = 47.5 \times 10^{-3} / (4 \times 1.732 \times 60 \times 0.1 \times 16.3) = 47.5 \times 10^{-3} / (0.678 \times 10^3) = 70 \mu\text{F}$$

$$\text{Valor comercial escolhido: } C = 100 \mu\text{F} // \quad (\text{obs.: } r = 7\%)$$

Questão 8


Quando $v_{in}(t) = -5 \text{ V}$, temos

$$v_{out}(t) = 2 - 0.7 = 1.3 \text{ V e portanto}$$


$$V_C = 1.3 - (-5) = 6.3 \text{ V. Quando } v_{in}(t) = 5 \text{ V,}$$

temos o diodo desligado e $v_{out}(t) = 5 + 6.3 = 11.3 \text{ V}$.


$$\text{Portanto, } V_{OC} = (1.3 + 11.3) / 2 = 6.3 \text{ V} //$$

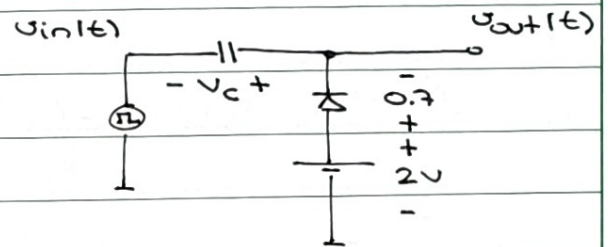

Questão 9

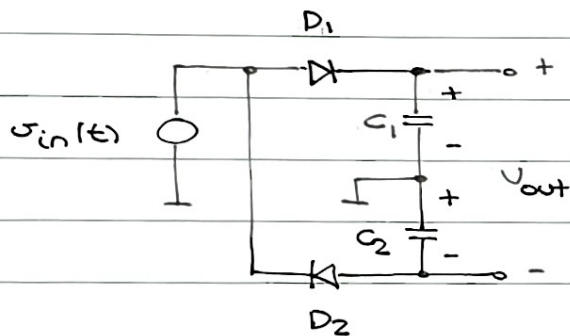


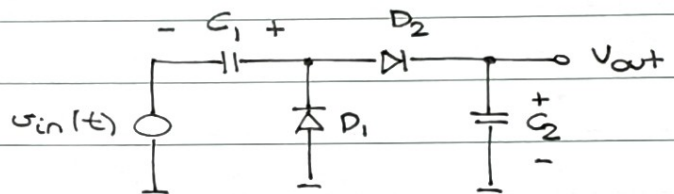Neste circuito, C_1 detecta o pico positivo de $v_{in}(t)$ e C_2 detecta o pico negativo. A diferença $V_p - (-V_p) = 2V_p$ aparece em V_{out} .



Neste circuito, o primeiro estágio (C_1 e D_1) desloca $v_{in}(t)$ V_p volts para cima, gerando uma forma de onda cujo pico superior está em $2V_p$. Esse valor de pico é detectado por C_2 e aparece em V_{out} .

Questão 10

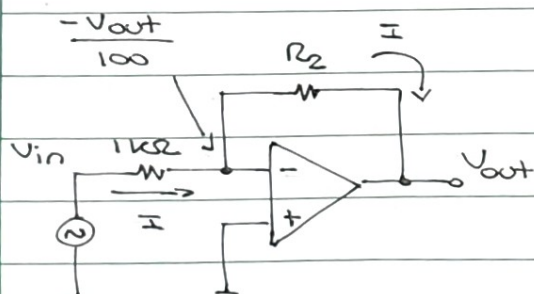

$$I = (V_{in} + (V_{out} / 100)) / 1000$$

$$V_{out} = -V_{out} / 100 - R_2 (V_{in} + (V_{out} / 100)) / 1000$$

$$\frac{V_{out}}{V_{in}} = \frac{-R_2 / 1000}{1 + (1 / 100) + (R_2 / 10^5)} = -5$$

$$-100 R_2 = -5.05 \times 10^5 - 5 R_2$$

$$95 R_2 = 5.05 \times 10^5 \rightarrow R_2 = 5316 \Omega //$$