



Aluno:

Prova Parcial #3 — Gabarito

Disciplina:

Eletrônica I

Turma:

2019/2

Professor:

José Gabriel

1

2

3

4

5

Questão ①

$$a) n_i = \frac{5.2 \times 10^{15} \times 350^{1.5}}{2.405 \times 10^{19}} \times \exp\left(\frac{-1.12 \times 1.6 \times 10^{-19}}{8.781 \times 10^{-9}} / (2 \times 1.38 \times 10^{-23} \times 350)\right) = 2.99 \times 10^{11} \text{ cm}^{-3}$$

$$p = 2.99^2 \times 10^{22} / 10^{17} = 8.94 \times 10^5 \text{ lacunas/cm}^3$$

$$b) J = 1.6 \times 10^{-19} \times (1350 \times 10^{17} + \underbrace{480 \times 8.94 \times 10^5}_{\text{desprezível}}) \times 10^5 = 2.16 \times 10^6 \text{ A/cm}^2$$

Questão ②

$$n_i = \frac{1.66 \times 10^{15} \times 300^{1.5}}{8.626 \times 10^{18}} \times \exp\left(\frac{-0.66 \times 1.6 \times 10^{-19}}{2.892 \times 10^{-6}} / (2 \times 1.38 \times 10^{-23} \times 300)\right) = 2.49 \times 10^{13} \text{ cm}^{-3}$$

$$p_n = 2.49^2 \times 10^{26} / 10^{16} = 6.222 \times 10^{10} \text{ lacunas/cm}^3$$

$$V_0 = \frac{1.38 \times 10^{-23} \times 300}{0.0259} \times \frac{\ln(10^{15} / (6.222 \times 10^{10}))}{9.685} = 0.251 \text{ V}$$

Questão ③

$$a) 1. (V_D = 0.7 \text{ V}) \rightarrow I_D = (10 - 2 \times 0.7) / 1000 = 8.6 \text{ mA}$$

$$V_D = 1.98 \times 0.026 \times \ln(8.6 \times 10^3 / (14.1 \times 10^{-9})) = 0.6858 \text{ V}$$

$$2. I_D = (10 - 2 \times 0.6858) / 1000 = 8.63 \text{ mA}$$

$$V_D = 1.98 \times 0.026 \times \ln(8.63 \times 10^3 / (14.1 \times 10^{-9})) = 0.6859 \text{ V}$$

$$3. I_D = (10 - 2 \times 0.6859) / 1000 = 8.63 \text{ mA}$$

$$b) 656 \text{ mV} \rightarrow 5 \text{ mA}$$

$$r_d = \Delta V / \Delta I = 36 / 5 = 7.2 \Omega$$

$$692 \text{ mV} \rightarrow 10 \text{ mA}$$

$$V_{D0} = 0.692 - 7.2 \times 0.01 = 0.62 \text{ V}$$

$$I_D = (10 - 2 \times 0.62) / (1000 + 2 \times 7.2) = 8.64 \text{ mA}$$

$$V_D = 0.62 + 7.2 \times 8.64 \times 10^{-3} = 0.682 \text{ V}$$


#### Questão (4)

Se o diodo DSN756 estiver desligado ( $-0.8 \text{ V} < v_{out}(t) < 8.2 \text{ V}$ ), então

$$v_{out}(t) = v_{in}(t) \times 1000 / (1000 + 100) = 10 v_{in}(t) / 11.$$

Se  $10 v_{in}(t) / 11 \geq 8.2 \text{ V}$ , ou seja,  $v_{in}(t) \geq 9.02 \text{ V}$ , então  $v_{out}(t) = 8.2 \text{ V}$ .

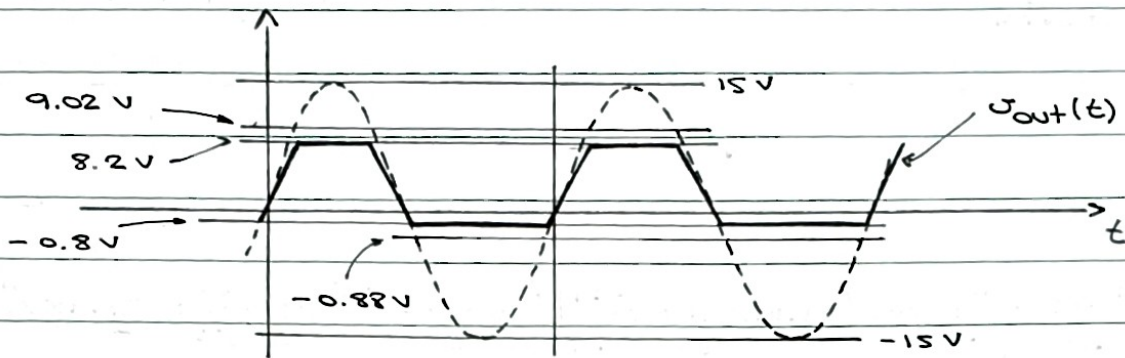Se  $10 v_{in}(t) / 11 \leq -0.8 \text{ V}$ , ou seja,  $v_{in}(t) \leq -0.88 \text{ V}$ , então  $v_{out}(t) = -0.8 \text{ V}$ .



#### Questão (5)

a)  $V_{AC, RMS} = 1 / \sqrt{2} = 0.707 \text{ V}$

$$V_{RMS} = \sqrt{10^2 + 0.707^2} = 10.025 \text{ V}$$

$$r = V_{AC, RMS} / V_{DC} = 0.0707 \text{ (ou seja, 7.1\%)}$$

Para que  $r = 15\%$ , precisamos de  $V_{DC} = V_{AC, RMS} / 0.15 = 0.707 / 0.15 = 4.71 \text{ V}$  /h

b)  $V_{AC, RMS} = 1 \text{ V}$

$$V_{RMS} = \sqrt{10^2 + 1} = 10.05 \text{ V}$$

$$r = V_{AC, RMS} / V_{DC} = 0.10 \text{ (ou seja, 10\%)}$$

Para que  $r = 15\%$ , precisamos de  $V_{DC} = V_{AC, RMS} / 0.15 = 1 / 0.15 = 6.67 \text{ V}$  /h

#### Questão (6)

a)  $(1 + \sqrt{3} r) V_{DC} = V_m \rightarrow r = ((19.3/18) - 1) / \sqrt{3} = 0.0417$

$$I_{DC} = 2\sqrt{3} \times 60 \times 100 \times 10^{-6} \times 19.3 \times 0.0417 = 0.0167 \text{ A}$$

$$R = 18 / I_{DC} = 1076 \Omega. \text{ Valor comercial imediatamente superior: } R = 1.2 \text{ k}\Omega$$
 /h

b)  $I_{DC} = 18 / 1200 = 0.015$

$$r = I_{DC} / (2\sqrt{3} \times 60 \times 100 \times 10^{-6} \times 19.3) = 0.0374$$

$$V_{DC} = 19.3 / (1 + \sqrt{3} \times 0.0374) = 18.13 \text{ V}$$

$$I_{DC} = 18.3 / 1200 = 0.0151$$

$$r = 0.0151 / (2\sqrt{3} \times 60 \times 100 \times 10^{-6} \times 19.3) = 0.0377$$

$$V_{DC} = 19.3 / (1 + \sqrt{3} \times 0.0377) = 18.12 \text{ V} / \text{(e, novamente, } I_{DC} = 0.0151 \text{ V)}$$
 /h