



Aluno(a):

Prova de Segunda Chamada — Gabarito

Disciplina:

Eletrônica I — EEL315

Turma:

2018-1

Professor(a):

José Gabriel

1

2

3

4

5

Questão ①

$$J_{tot} = 1.6 \times 10^{-19} \left( \frac{34 \times (-9 \times 10^{16})}{3 \times 10^{-4}} - \frac{12 \times 3 \times 10^{16}}{3 \times 10^{-4}} \right) = -1.6 \times 114 \times 10 = -1.824 \times 10^3 \text{ A/cm}^2$$

$$I_{dif} = J_{tot} \cdot A \Rightarrow I_{dif} = -1.824 \times 10^3 \times \frac{(500 \times 10^{-7})^2}{25 \times 10^{-10} \text{ cm}^2} \Rightarrow I_{dif} = -4.56 \text{ mA}$$

Questão ②

$$n_i = 5.2 \times 10^{15} \times (350)^{3/2} \exp\left(\frac{-1.12 \times 1.6 \times 10^{-19}}{(2 \times 1.38 \times 10^{-23} \times 350)}\right) = 0.18551 \times 100 = 18.551$$

$$n_i = 5.2 \times 10^{15} \times 6.548 \times 10^3 \times 8.778 \times 10^{-9} = 299 \times 10^9 = 2.99 \times 10^{11} / \text{cm}^3$$

$$V_D = \frac{1.38 \times 10^{-23} \times 350 \ln\left(\frac{10^{17} \times 10^{17}}{(2.99)^2 \times 10^{22}}\right)}{1.6 \times 10^{-19}} \Rightarrow V_D = 768 \text{ mV}$$

30.19 mV      25.44

Questão ③

$$I_D = 10^{-15} \exp(V_D / 0.028) \quad (a) \quad \text{Chute inicial: } V_D = 0.4 \text{ V}$$

$$V_D = (0.9 - 2200 I_D) / 2 \quad (b)$$

Iteração ①  $V_D = 0.4 \text{ V} \xrightarrow{(a)} I_D = 4.802 \text{ nA} \xrightarrow{(b)} V_D = 0.45 \text{ V}$

Iteração ②  $V_D = 0.45 \text{ V} \xrightarrow{(a)} I_D = 32.88 \text{ nA} \xrightarrow{(b)} V_D = 0.45 \text{ V}$

Questão ④

$$\frac{12 - V_Z}{1200} = \frac{V_Z}{12000} + \frac{V_Z - 8.1}{5}$$


$$120 - 10 V_Z = V_Z + 2400 V_Z - 2400 \times 8.1$$

$$2411 V_Z = 19560$$

$$V_Z = 8.113 \text{ V}$$

$$I_Z = 2.6 \text{ mA}$$

(modelagem: ver PF)

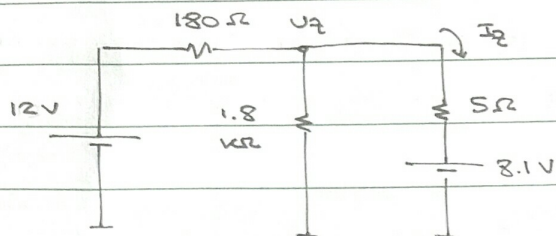

$$\frac{12 - V_Z}{180} = \frac{V_Z}{1800} + \frac{V_Z - 8.1}{5}$$


$$120 - 10V_Z = V_Z + 360V_Z - 360 \times 8.1$$

$$371V_Z = 3036$$

$$V_Z = 8.183 \text{ V}$$

$$I_Z = 16.6 \text{ mA}$$

Questão 5

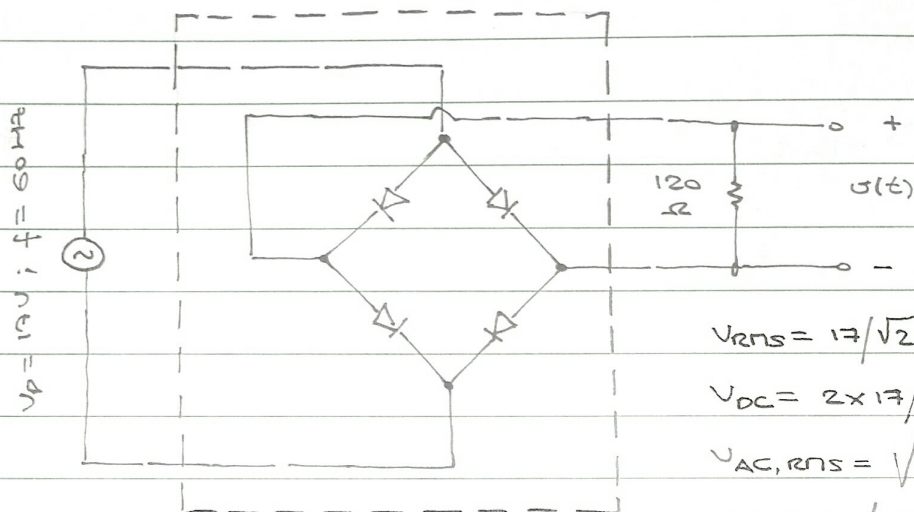

$$V_{RMS} = 17/\sqrt{2} = 12.02 \text{ V}$$

$$V_{DC} = 2 \times 17/\pi = 10.83 \text{ V}$$

$$V_{AC, RMS} = \sqrt{12.02^2 - 10.83^2} = 5.21 \text{ V}$$

$$r = 5.21/10.83$$

$$P = 12.02^2/120 \Rightarrow P = 1.2 \text{ W} \quad (1.2 \text{ W})$$

$$r = 48\%$$

Questão 6

$$(1 + \sqrt{3} \times 0.15) V_{DC} = 17 \rightarrow V_{DC} = 13.55 \text{ V}$$

$$I_{DC} = 13.55/120 = 113 \text{ mA}$$

$$C = \frac{113 \times 10^{-3}}{\frac{4 \times 1.7 \times 60 \times 0.15 \times 17}{1.04 \times 10^3}} = \frac{113 \times 10^{-6}}{1.04} = 109 \mu\text{F}$$

Menor capacitância utilizável (valor comercial):

$$C = 220 \mu\text{F}$$

Obs.: com  $C = 220 \mu\text{F}$ , temos  $r = 113 \times 10^{-3} / (4 \times 1.7 \times 60 \times 0.22 \times 10^{-3} \times 17)$

$$\Rightarrow r = 113/1526 = 7.4\% \Rightarrow V_{DC} = 17 / (1 + \sqrt{3} \times 0.074) = 15.1 \text{ V}$$

$$\Rightarrow I_{DC} = 126 \text{ mA} \Rightarrow r = 126/113 \times 7.4 \Rightarrow r = 8.3\% \text{ (ou)}$$

Obs. 2: com  $C = 100 \mu\text{F}$ , temos  $r = 113 \times 10^{-3} / (4 \times 1.7 \times 60 \times 0.1 \times 10^{-3} \times 17) = 13.3\%$

$$\Rightarrow r = 113/694 = 16.3\% \Rightarrow V_{DC} = 17 / (1 + \sqrt{3} \times 0.163) = 13.3 \text{ V}$$

$$\Rightarrow I_{DC} = 111 \text{ mA} \Rightarrow r = 111/113 \times 16.3 \Rightarrow r = 16\% \text{ (> 15\% !)}$$

Questão 7

Chute inicial :  $r_{\text{capacitor}} = 2\% \Rightarrow V_{DC} = 17 / (1 + \sqrt{3} \times 0.02) = 16.4 \text{ V}$

$I_{DC} = \frac{16.4}{120} + \frac{16.4 - 8.2}{120} = 205 \text{ mA}$

$r_{\text{capacitor}} = 205 \times 10^{-3} / (4 \times 1.7 \times 60 \times 0.68 \times 10^{-3} \times 17) = 205 / 4716 = 0.043$


$V_{DC} = 17 / (1 + \sqrt{3} \times 0.043) = 15.8 \text{ V}$

$I_{DC} = \frac{15.8}{120} + \frac{15.8 - 8.2}{120} = 195 \text{ mA}$


$r_{\text{capacitor}} = 195 / 205 \times 0.043 = 4.1\%$

$r_{RL} = 0.041 \times \frac{5}{120+5} \times \frac{15.8}{8.2} \Rightarrow \boxed{r_{RL} = 0.32\%}$

Questão 8

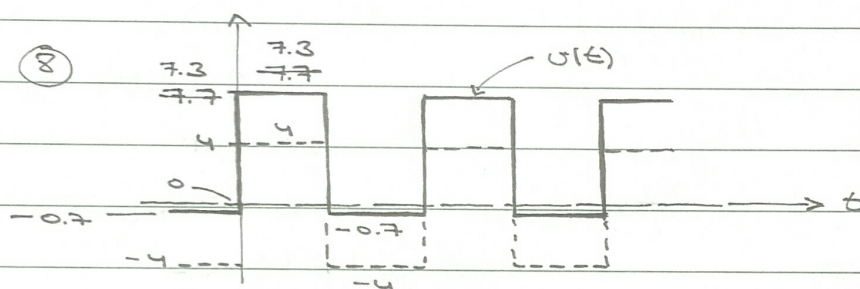

Questão 9

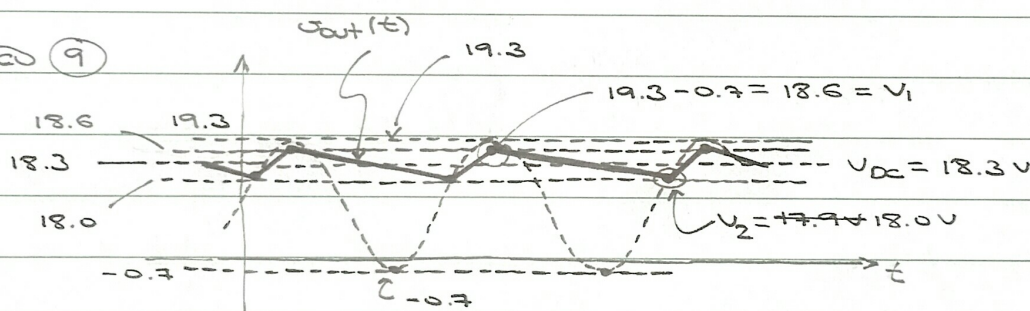

$V_{DC} \approx 15 \text{ V (chute inicial)} \Rightarrow r = (15 / 4700) / (4 \times 1.7 \times 30 \times 0.1 \times 10^{-3} \times 18.6)$

$r = 3.2 / 379 = 0.8\% \Rightarrow V_{DC} = 18.6 / (1 + \sqrt{3} \times 0.008) = 18.4 \text{ V}$

$r = 18.4 / 15 \times 0.8 \Rightarrow r = 1\% \Rightarrow V_{DC} = 18.6 / (1 + \sqrt{3} \times 0.01) = 18.3 \text{ V}$

Questão 10

$V_x + 10^3 \left( \frac{V_x}{10^3} - \frac{(V_{in} - V_x)}{10^4} \right) = 1000 (V_{in} - V_x)$

$V_x + V_x - 0.1 V_{in} + 0.1 V_x = 1000 V_{in} - 1000 V_x$

$1002.1 V_x = 1000.1 V_{in}$

$V_x = (1000.1 / 1002.1) V_{in}$

$V_{out} = 1000 \left( V_{in} - \frac{1000.1}{1002.1} V_{in} \right)$

$V_{out} / V_{in} = 20000 / 10021 \Rightarrow$

$\boxed{V_{out} / V_{in} = 1.9958}$

