



Aluno(a):

Prova Final 2018-2 — Gabarito

Disciplina:

Eletrônica I


Turma:

2018/2

Professor(a):

José Gabriel

Questão ①

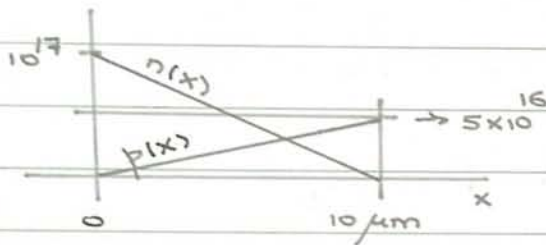

$$dn/dx = -10^{17} / (10 \times 10^{-4}) = -10^{20} / \text{cm}^4$$

$$dp/dx = (5 \times 10^{16}) / (10 \times 10^{-4}) = 5 \times 10^{19} / \text{cm}^4$$

$$J = 1.6 \times 10^{-19} (-34 \times 10^{20} - 12 \times 5 \times 10^{19}) = -640 \text{ A/cm}^2$$

$$I = J \cdot A = -640 \times 500 \times 10^{-7} \times 500 \times 10^{-7} = \boxed{1.6 \mu\text{A}}$$

$$(6.4 \times 25 \times 10^6 \times 10^{-14} = 160 \times 10^{-8} \text{ A})$$

Questão ②

$$n_i = \frac{1.66 \times 10^{15} (400)^{3/2}}{1.328 \times 10^{19}} \exp\left(\frac{-0.66 \times 1.6 \times 10^{-19}}{2 \times 1.38 \times 10^{-23} \times 400}\right) = 9.3146 \times 10^{14} / \text{cm}^3$$

$$1.328 \times 10^{19}$$


$$\frac{-1.056 \times 10^4}{2.76 \times 4 \times 100} = \frac{-105.6}{11.04} = -9.565 \quad (e^{-9.565} = 7.01 \times 10^{-5})$$

$$V_0 = \frac{1.38 \times 10^{-23} \times 400}{1.6 \times 10^{-19}} \ln\left(\frac{2 \times 10^{17} \times 5 \times 10^{16}}{9.3146^2 \times 10^{28}}\right) = 34.5 \times 9.352 = \boxed{323 \text{ mV}}$$

$$34.5 \text{ mV}$$

$$\frac{100 \times 10^4}{86.762} = 1.1526 \times 10^4 \quad (\ln(1.1526 \times 10^4) = 9.352)$$

Questão ③

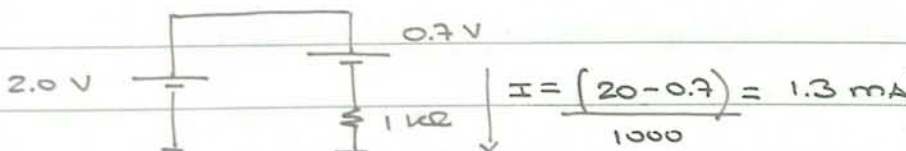


> Então, vamos escolher um modelo linear para correntes em torno de 1.3 mA.

$$573 \text{ mV} \rightarrow 1 \text{ mA} \rightarrow r_d = (692 - 573) / (10 - 1) = 119 / 9 = 13.2 \Omega$$

$$692 \text{ mV} \rightarrow 10 \text{ mA} \quad V_{D0} + 13.2 \times 10 \times 10^{-3} = 0.692 \text{ V} \rightarrow V_{D0} = 0.56 \text{ V}$$

Usando o modelo V_{D0}, r_d :

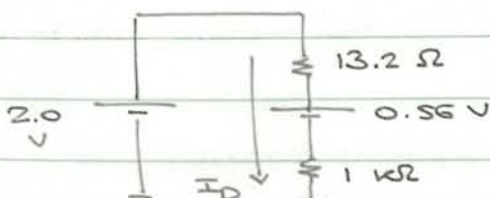

$$I_D = \frac{2 - 0.56}{1013.2} \rightarrow \boxed{I_D = 1.42 \text{ mA}}$$

Questão (4)

Chute inicial: $V_D = 0.7 \text{ V} \rightarrow I_D = (2 - V_D) / 1000 = 1.3 \text{ mA}$

Iteração 1: $V_D = 1.98 \times 0.026 \times \ln((1.3 \times 10^{-3}) / (1.41 \times 10^{-8})) = 0.588 \text{ V}$

$I_D = (2 - 0.588) / 1000 = 1.412 \text{ mA}$ $\leftarrow (\ln(92200) = 11.43)$



Iteração 2: $V_D = 1.98 \times 0.026 \times \ln((1.412 \times 10^{-3}) / (1.41 \times 10^{-8})) = 0.593 \text{ V}$

$I_D = (2 - 0.593) / 1000 = 1.407 \text{ mA}$ $\leftarrow (\ln(100142) = 11.51)$

Iteração 3: $V_D = 1.98 \times 0.026 \times \ln((1.407 \times 10^{-3}) / (1.41 \times 10^{-8})) = 0.593 \text{ V}$

$I_D = (2 - 0.593) / 1000 = \boxed{1.407 \text{ mA}}$ $\leftarrow (\ln(99787) = 11.51)$

Questão (5):

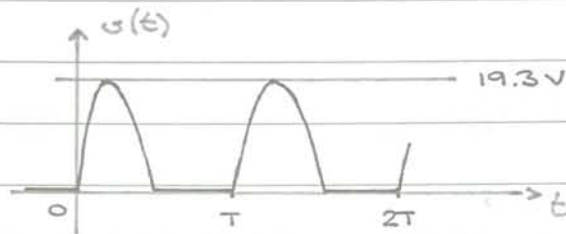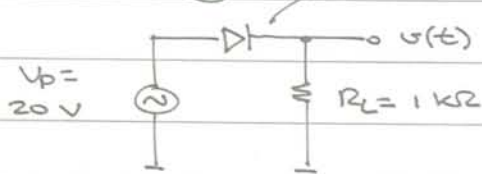

$V_{RMS} = 19.3 / 2 = 9.65 \text{ V}$

$V_{AC, RMS} = \sqrt{9.65^2 - 6.15^2} = 7.44 \text{ V}$

$V_{DC} = 19.3 / \pi = 6.15 \text{ V}$

$r = 7.44 / 6.15 \Rightarrow \boxed{r = 1.21} \approx \boxed{121\%}$

Questão (6)

$(1 + \sqrt{3} \times 0.05) V_{DC} = 19.3 \rightarrow V_{DC} = 17.8 \text{ V} \rightarrow I_{DC} = 17.8 \text{ mA}$

$C = \frac{17.8 \times 10^{-3}}{2 \times 1.7 \times 60 \times 0.05 \times 19.3} = \frac{17.8 \times 10^{-3}}{197} = 90 \mu\text{F} \rightarrow \boxed{C = 100 \mu\text{F}}$

Usando $C = 100 \mu\text{F}$, temos $r = \frac{17.8 \times 10^{-3}}{2 \times 1.7 \times 60 \times 19.3 \times 0.1 \times 10^{-3}} = \frac{17.8}{394} = 4.5\%$

$V_{DC} = 19.3 / (1 + \sqrt{3} \times 0.045) \rightarrow V_{DC} = 17.9 \text{ V} \rightarrow I_{DC} = 17.9 \text{ mA} \rightarrow r = \frac{17.9}{394} = \boxed{4.5\%}$

Questão (7)

Chute inicial: $r = 10\% \rightarrow (1 + \sqrt{3} \times 0.1) V_{DC} = 16.3 \rightarrow V_{DC} = 13.9 \text{ V}$

Então: $I_{DC} = (13.9 - 8.2) / 180 = 32 \text{ mA}$

$r = \frac{32 \times 10^{-3}}{4 \times 1.7 \times 60 \times 16.3 \times 0.33 \times 10^{-3}} = \frac{32}{2194} = 1.5\%$

Repetindo: $r = 1.5\% \rightarrow (1 + \sqrt{3} \times 0.015) V_{DC} = 16.3 \rightarrow V_{DC} = 15.9 \text{ V}$

$I_{DC} = (15.9 - 8.2) / 180 = 43 \text{ mA} \rightarrow r = 43 / 2194 = 2\%$

$(1 + \sqrt{3} \times 0.02) V_{DC} = 16.3 \rightarrow V_{DC} = 15.8 \text{ V} \rightarrow I_{DC} = \frac{15.9 - 8.2}{180} = 42 \text{ mA}$

Agora que sabemos que $r = 2\%$ (capacitor) e $V_{DC} = 15.8 \text{ V}$, só falta encontrar r_2 .


$$I_{RL} = 8.2 / 330 = 25 \text{ mA}$$

$$I_z = I_{oc} - I_{RL} = 42 \text{ mA} - 25 \text{ mA} = 17 \text{ mA}$$



Usando pontos próximos de 17 mA na Tabela 3: $r_z = \frac{8.2 - 8.161}{0.02 - 0.01} = 3.9 \Omega$

Então: $r_{zL} = 2\% \times \frac{3.9}{183.9} \times \frac{15.8}{8.2} \Rightarrow \boxed{r = 0.08\%}$


Questão 8

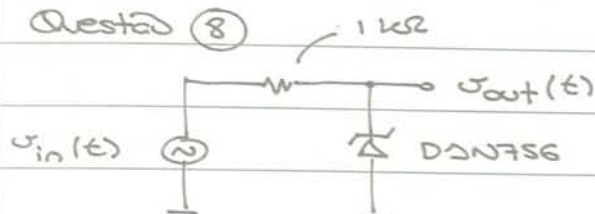


Item opcional:

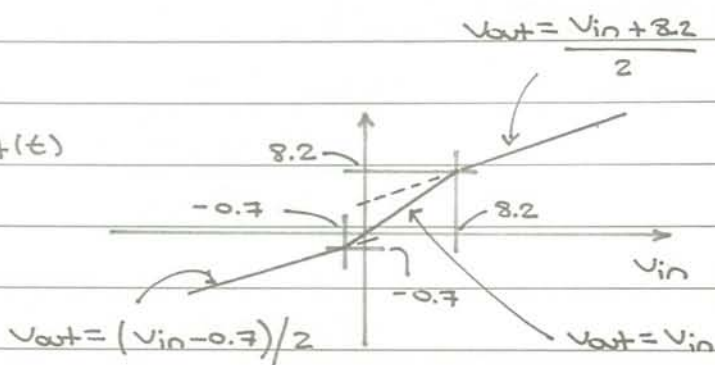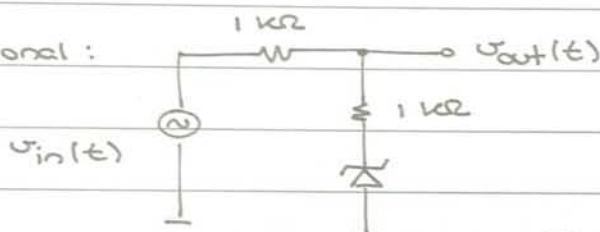

Questão 9

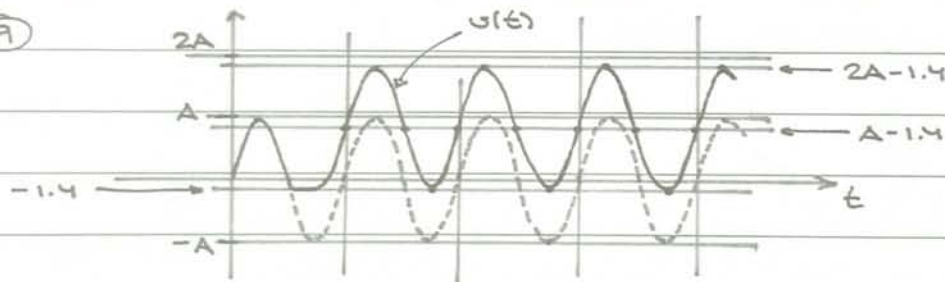

Questão 10

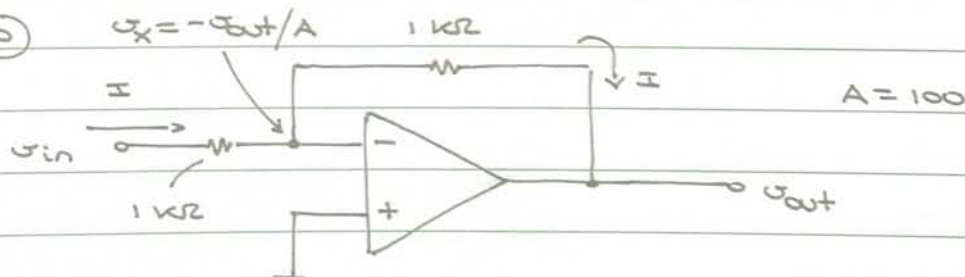

$$I = \frac{v_{in} + \frac{v_{out}}{A}}{1000}$$

$$v_{out} = -\frac{v_{out}}{A} - 1000 \left(\frac{v_{in} + \frac{v_{out}}{A}}{1000} \right) \Rightarrow v_{out} \left(1 + \frac{1}{A} + \frac{1}{A} \right) = -v_{in}$$

$A = 100 \Rightarrow \frac{v_{out}}{v_{in}} = \frac{-1}{1 + \frac{2}{100}} = \frac{-1}{1.02} \Rightarrow \boxed{\frac{v_{out}}{v_{in}} = -0.98}$