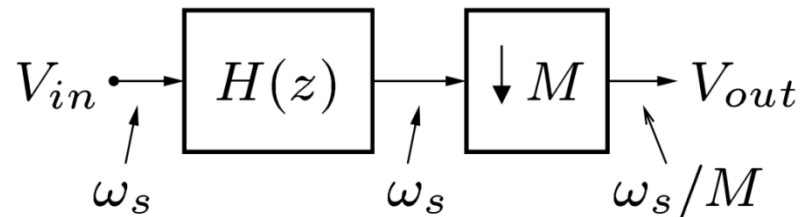


Analog Decimation Filters

A. Petraglia
Universidade Federal do Rio de Janeiro
DEL, COPPE

Decimation and Interpolation Filters

Decimation Filter







Ideal Frequency Response


$$H(e^{j\omega}) = \begin{cases} 1, & |\omega| \leq \omega_s/2M \\ 0, & \omega_s/2M < |\omega| \leq \omega_s/2 \end{cases}$$

- The cascade of a lowpass filter and a down-sampler is called a *decimation filter*;
- Filter $H(z)$ attenuates input frequency components greater than $\omega_s/2M$;
- The sampling rate can then be reduced by the factor M .

Sampling of Analog Signals

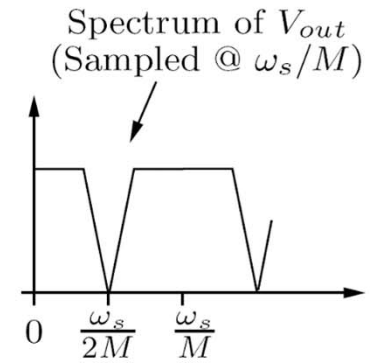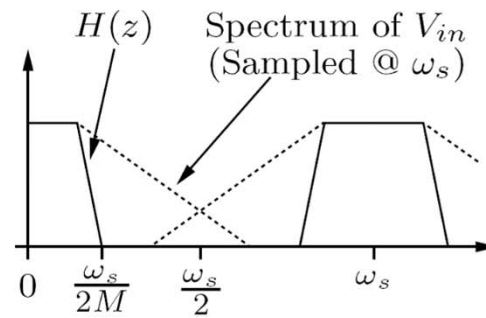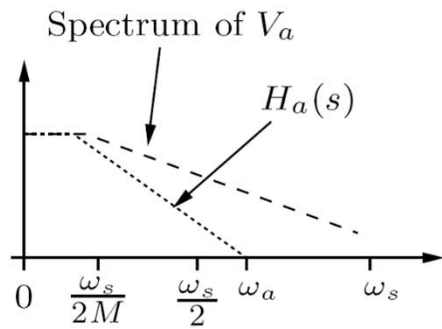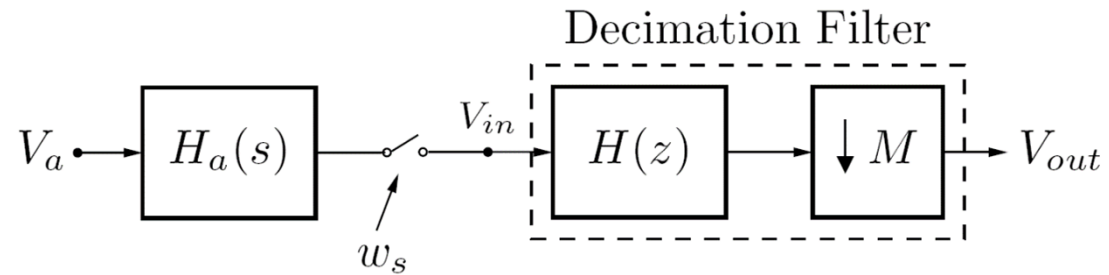

Sampling of Analog Signals

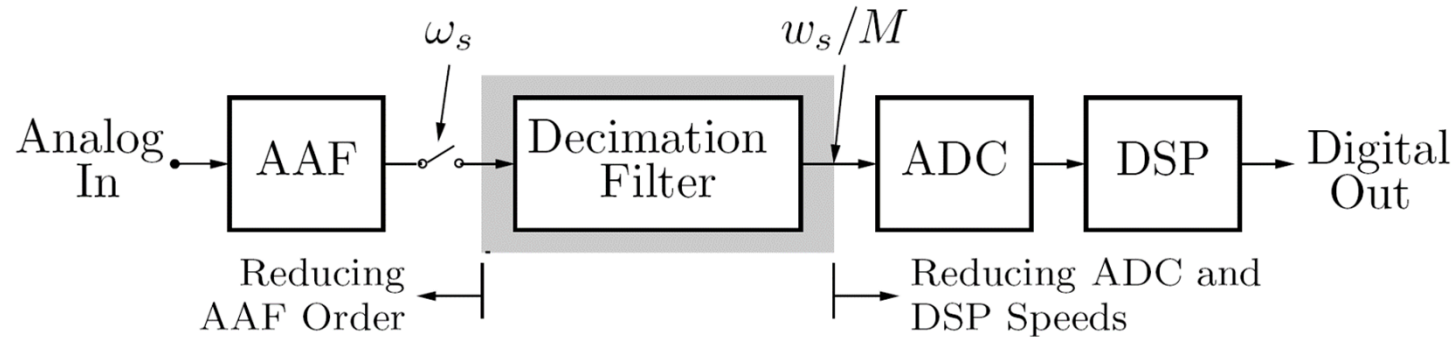

- Output of the anti-aliasing filter (AAF) is oversampled by factor M :
→ transition band of AAF can be increased;
- Accurate bandlimiting provided by SC filter $H(z)$ allows sampling rate reduction:
→ reduction of ADC and DSP power consumption.

Efficient Decimation Filter Design

FIR Decimation Filters

$$\begin{aligned} H(z) &= h(0) + h(1)z^{-1} + h(2)z^{-2} + \dots + h(7)z^{-7} \\ &= \underbrace{h(0) + h(3)z^{-3} + h(6)z^{-6}}_{H_0(z^3)} + z^{-1} \underbrace{(h(1) + h(4)z^{-3} + h(7)z^{-6})}_{H_1(z^3)} + z^{-2} \underbrace{(h(2) + h(5)z^{-3})}_{H_2(z^3)} \\ &= H_0(z^3) + z^{-1}H_1(z^3) + z^{-2}H_2(z^3) \end{aligned}$$


In the general case:

$$H(z) = \sum_{n=0}^{N-1} h(n)z^{-n} = \sum_{k=0}^{M-1} z^{-k} H_k(z^M)$$

Efficient Decimation Filter Design

FIR Decimation Filters
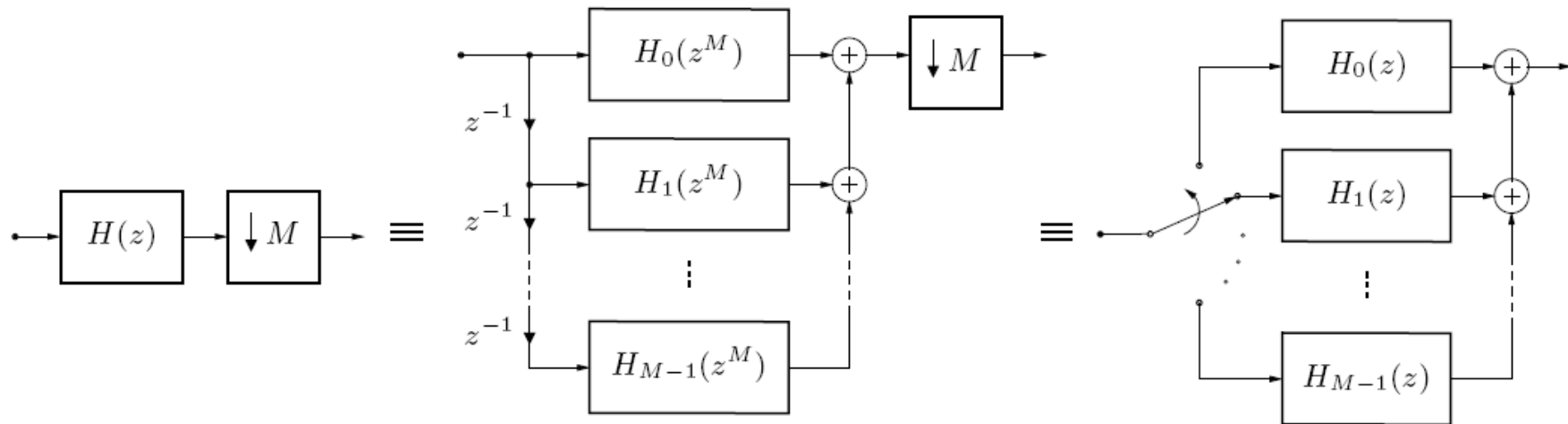
$$H(z) = \sum_{n=0}^{N-1} h(n)z^{-n} = \sum_{k=0}^{M-1} z^{-k} H_k(z^M)$$




Efficient Decimation Filter Design

IIR Decimation Filters

$$H(z) = \frac{A(z)}{B(z)} = \frac{A(z)P(z)}{B(z)P(z)} = \frac{Q(z)}{D(z^M)} = \frac{\sum_{k=0}^{M-1} z^{-k} Q_k(z^M)}{D(z^M)}$$
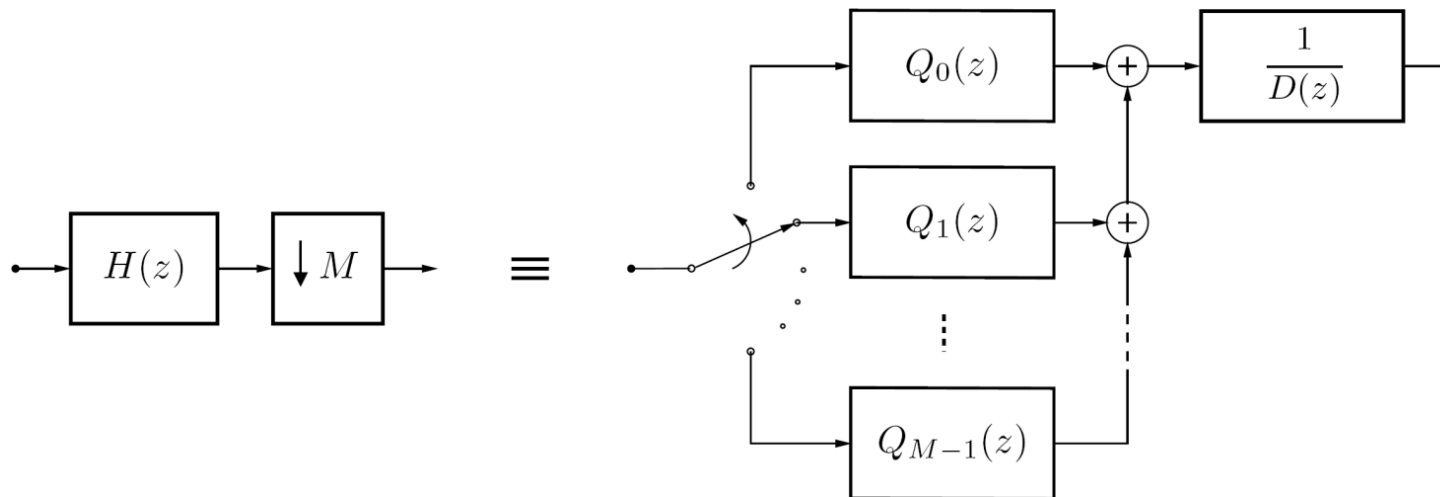
$$H(z) = \sum_{k=0}^{M-1} z^{-k} H_k(z^M) \quad H_k(z) = \frac{Q_k(z)}{D(z)}$$



Efficient Decimation Filter Design

Design Example


- passband edge frequency = 2.5 MHz
- stopband edge frequency = 4.5 MHz
- passband ripple < 0.4 dB
- stopband attenuation > 25 dB
- Decimation factor $M = 3$
- Input sampling rate = 30 MHz

Efficient Decimation Filter Design


The filter transfer function has been designed with 6 zeros and 2 poles

- low sensitivity to coefficient errors -> small capacitance spread
- small circuit complexity -> low power consumption

Before down-sampling

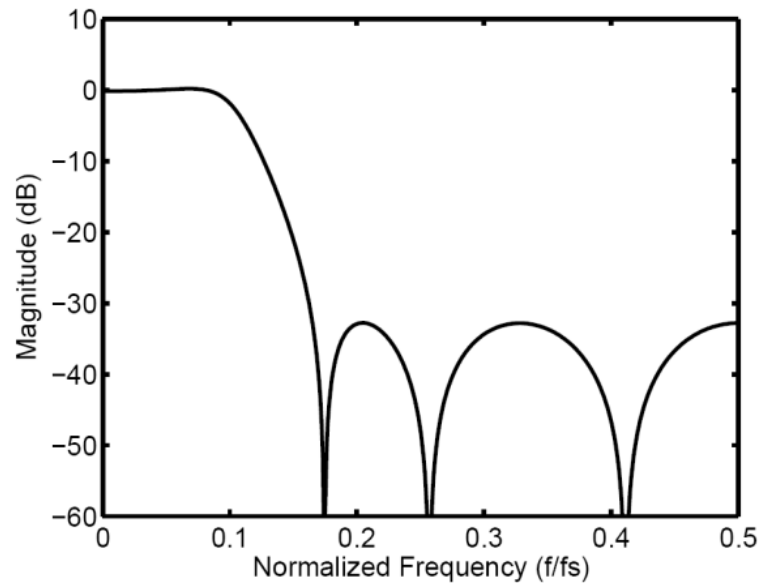

After down-sampling

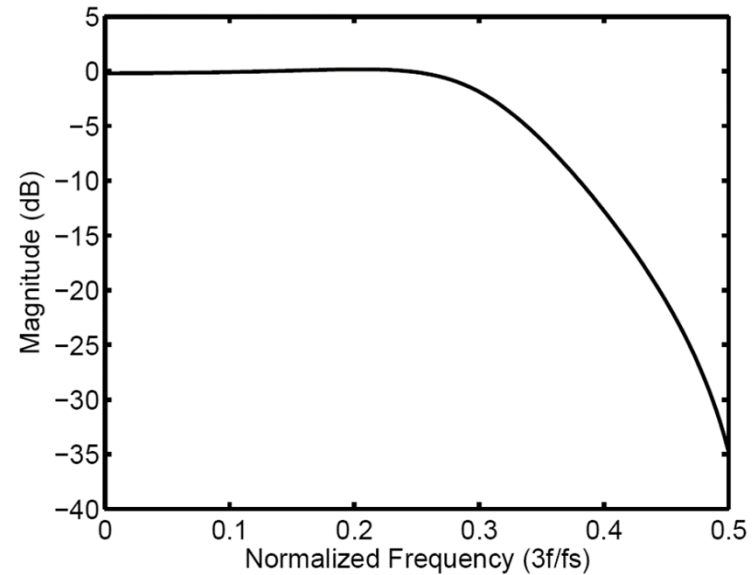

Efficient Decimation Filter Design

The filter transfer function has been designed with 6 zeros and 2 poles:

$$\begin{aligned} a_0 &= 0.0405 \\ a_1 &= 0.0353 \\ a_2 &= 0.0615 \\ a_3 &= 0.0651 \\ a_4 &= 0.0615 \\ a_5 &= 0.0353 \\ a_6 &= 0.0405 \\ \\ b_0 &= 1.0000 \\ b_1 &= -1.3166 \\ b_2 &= 0.6631 \end{aligned}$$
$$H(z) = \frac{A(z)}{B(z)} = \frac{A(z)P(z)}{B(z)P(z)} = \frac{Q(z)}{D(z^M)} = \frac{\sum_{k=0}^{M-1} z^{-k} Q_k(z^M)}{D(z^M)}$$
$$P(z) = 1 + 1.317z^{-1} + 1.070z^{-2} + 0.873z^{-3} + 0.4397z^{-4}$$
$$B(z)P(z) = 1 + 0.3369z^{-3} + 0.2915z^{-6}$$
$$D(z) = 1 + 0.3369z^{-1} + 0.2915z^{-2}$$


Efficient Decimation Filter Design

Coefficients of the polyphase components:

$H(z)$	$Q_k(z)$	$D(z)$
$a_0 = 0.0405$	$q_{00} = 0.0405$	$d_0 = 1.0000$
$a_1 = 0.0353$	$q_{01} = 0.2192$	$d_1 = 0.3369$
$a_2 = 0.0615$	$q_{02} = 0.2366$	$d_2 = 0.2915$
$a_3 = 0.0651$	$q_{03} = 0.0509$	
$a_4 = 0.0615$	$q_{10} = 0.0886$	
$a_5 = 0.0353$	$q_{11} = 0.2616$	
$a_6 = 0.0405$	$q_{12} = 0.1734$	
$b_0 = 1.0000$	$q_{13} = 0.0178$	
$b_1 = -1.3166$	$q_{20} = 0.1513$	
$b_2 = 0.6631$	$q_{21} = 0.2550$	
	$q_{22} = 0.1012$	



Efficient Decimation Filter Design

Block diagram of the decimation filter

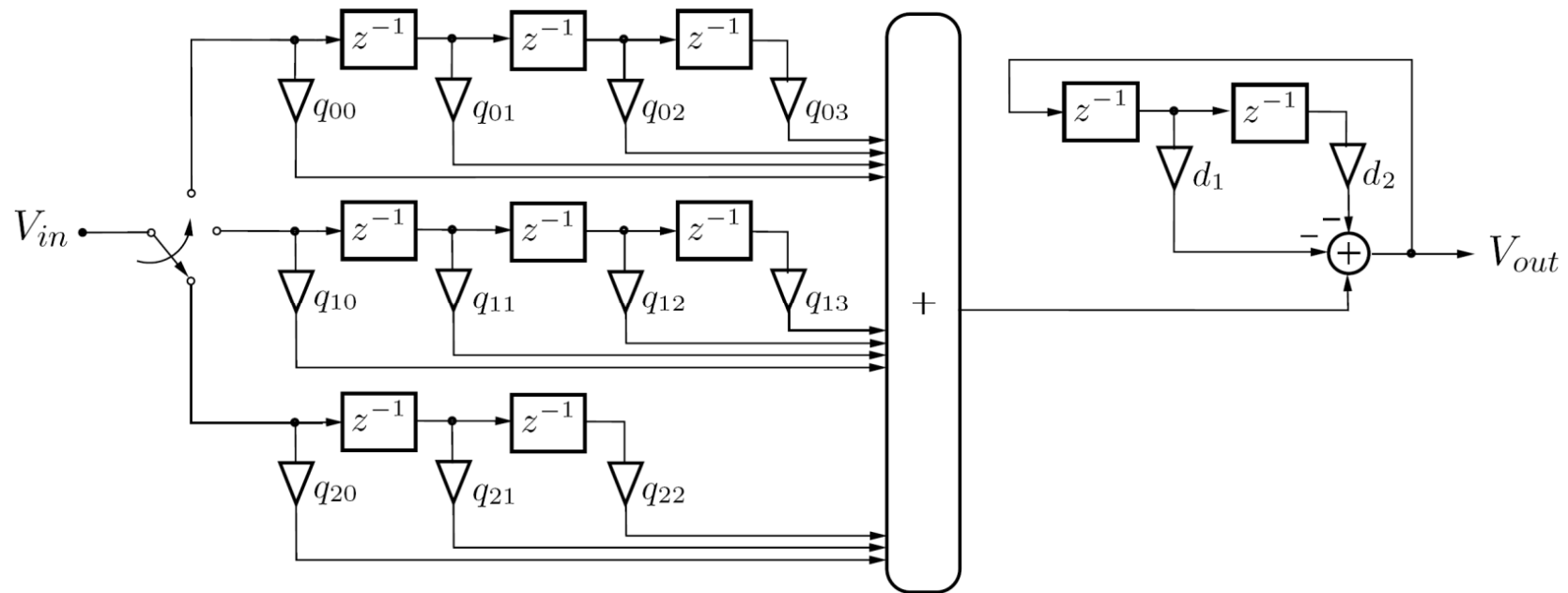

Efficient Decimation Filter Design

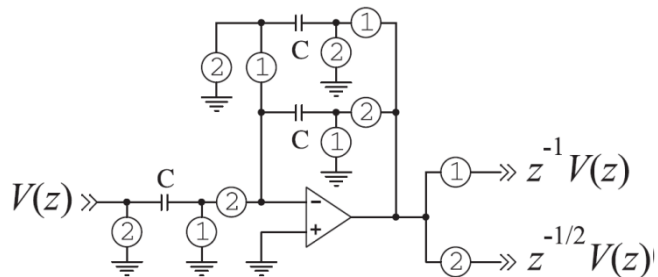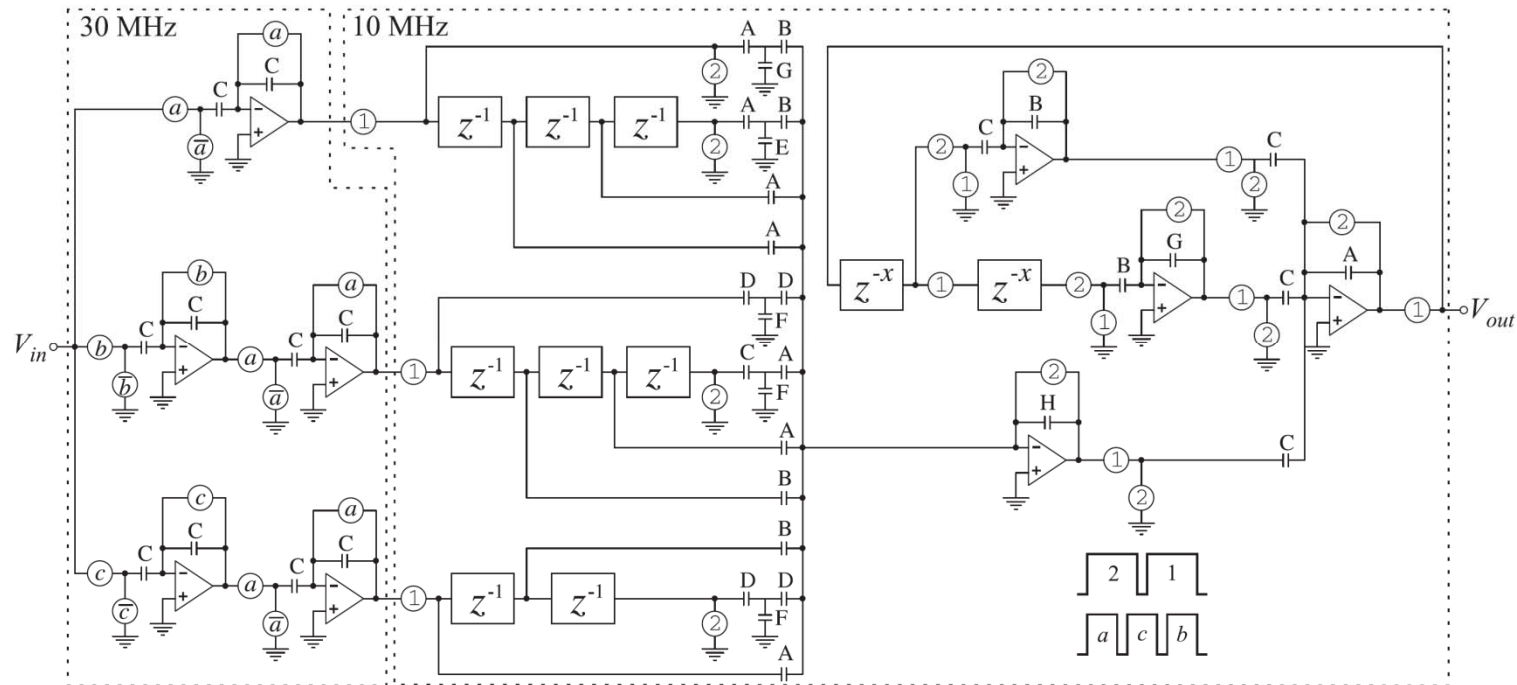
Schematic diagram of the decimation filter



$A = 0.2 \text{ pF}$	$E = 0.7 \text{ pF}$
$B = 0.3 \text{ pF}$	$F = 0.8 \text{ pF}$
$C = 0.1 \text{ pF}$	$G = 0.9 \text{ pF}$
$D = 0.4 \text{ pF}$	$H = 1.2 \text{ pF}$

Efficient Decimation Filter Design

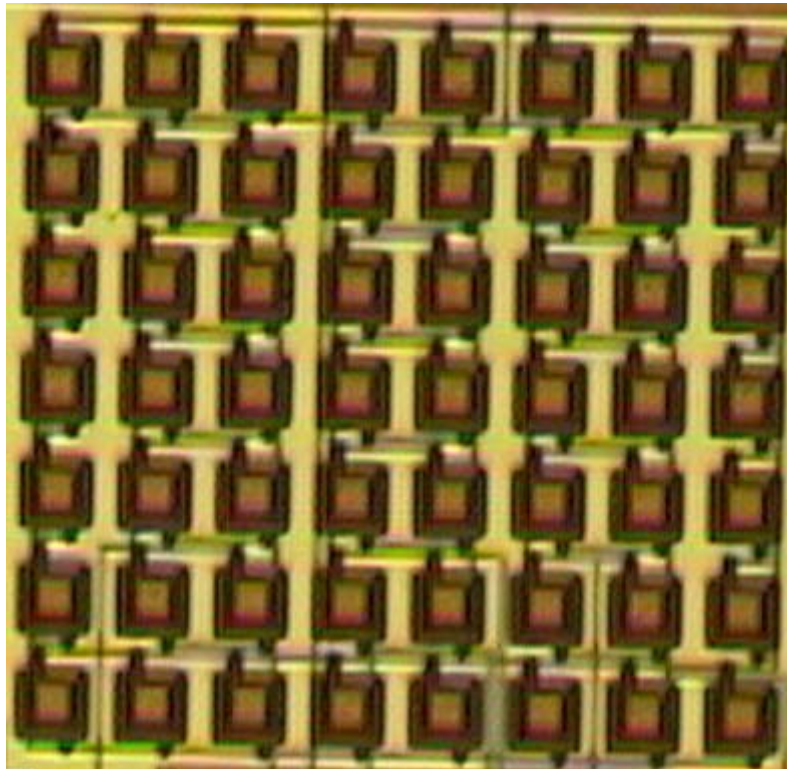
Capacitances are implemented by parallel associations of identical 0.1 pF units



A = 0.2 pF	E = 0.7 pF
B = 0.3 pF	F = 0.8 pF
C = 0.1 pF	G = 0.9 pF
D = 0.4 pF	H = 1.2 pF


Efficient Decimation Filter Design

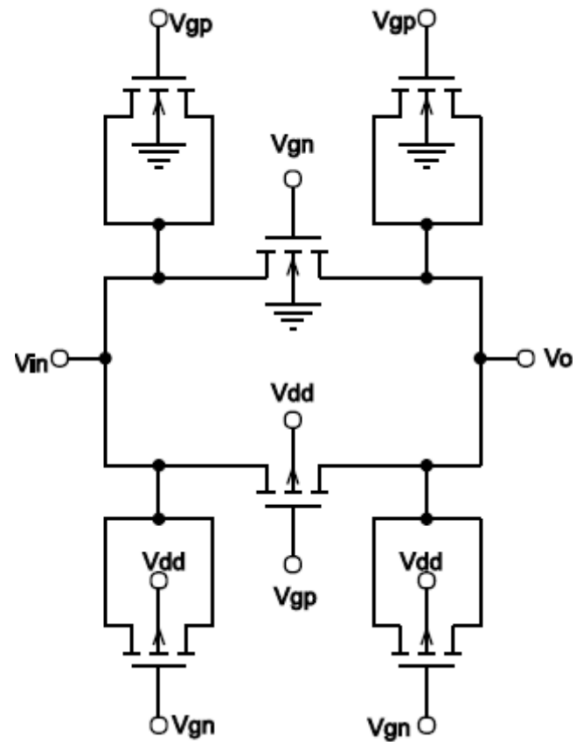Switches are implemented with dummy transistors to reduce charge injection




Efficient Decimation Filter Design

Operational transconductance amplifiers

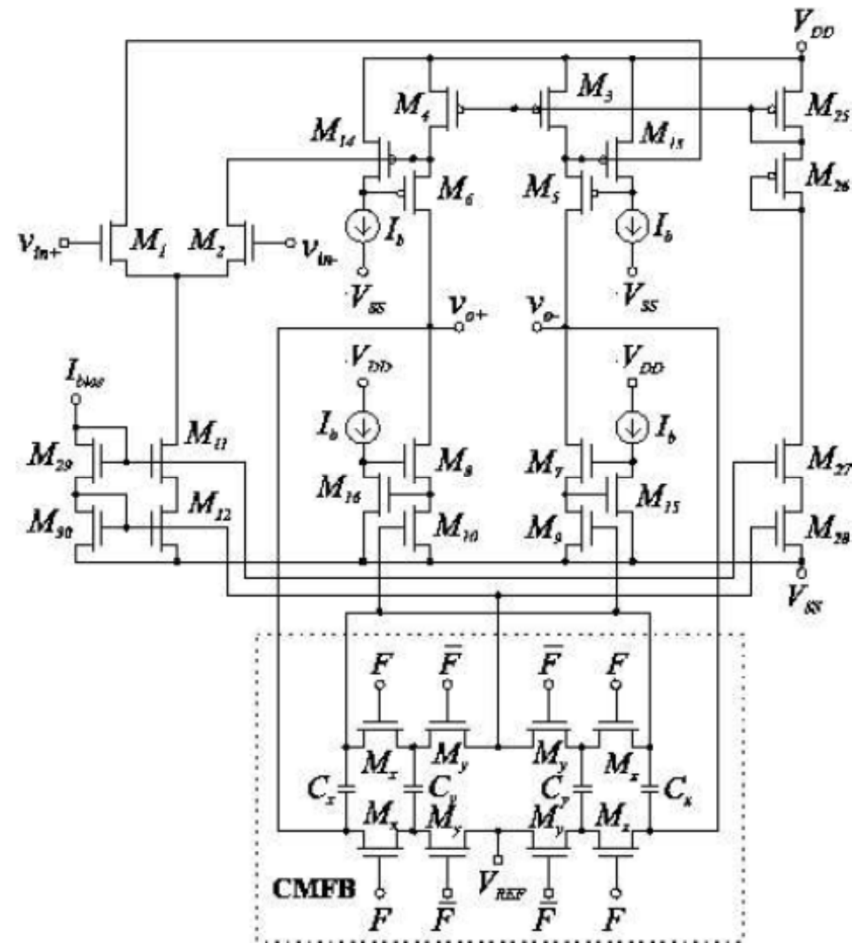


Efficient Decimation Filter Design

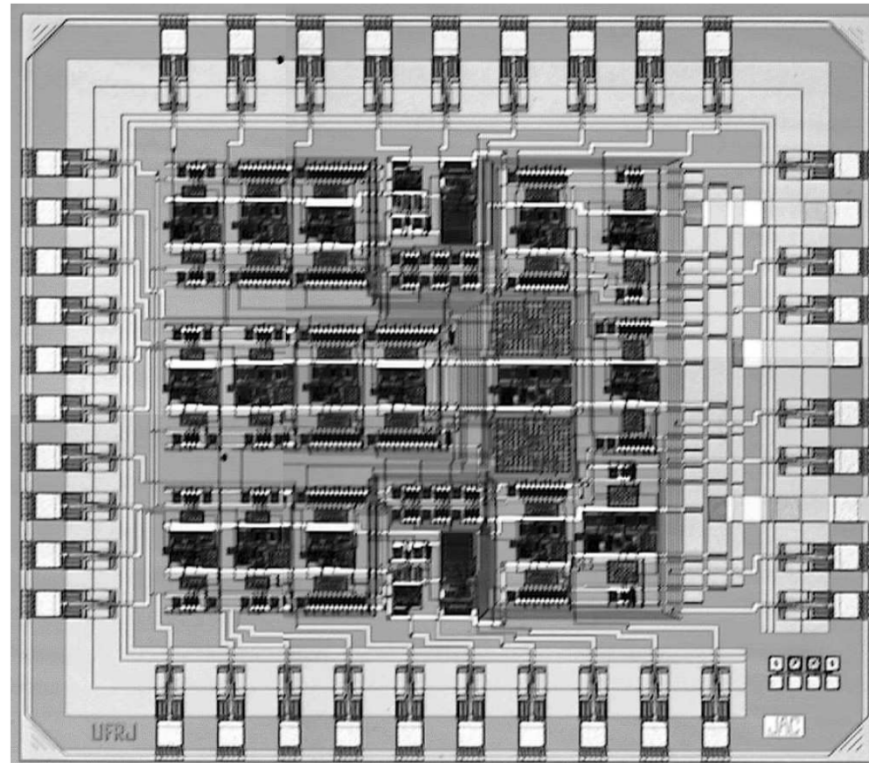

Chip photograph – Die area = $1.86 \times 1.50 \text{ mm}^2$


Efficient Decimation Filter Design

Measured and ideal frequency responses

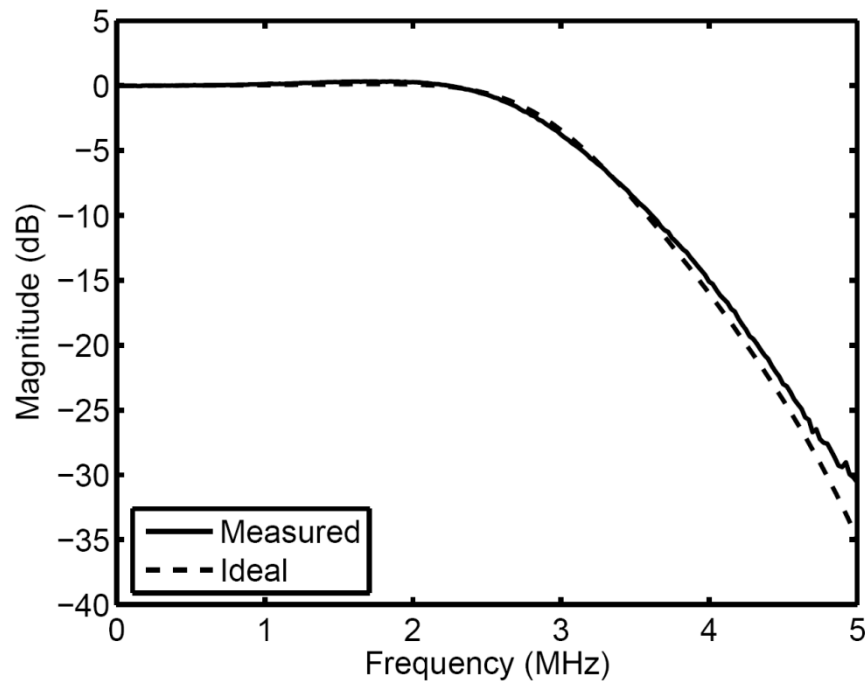

Voltage Supply	5V
Input Sampling Frequency	30 MHz
Output Sampling Frequency	10 MHz
Dynamic Range (1% THD)	58 dB
Dye Area	2.8 mm ²
Power Consumption	67.2 mW

Efficient Decimation Filter Design

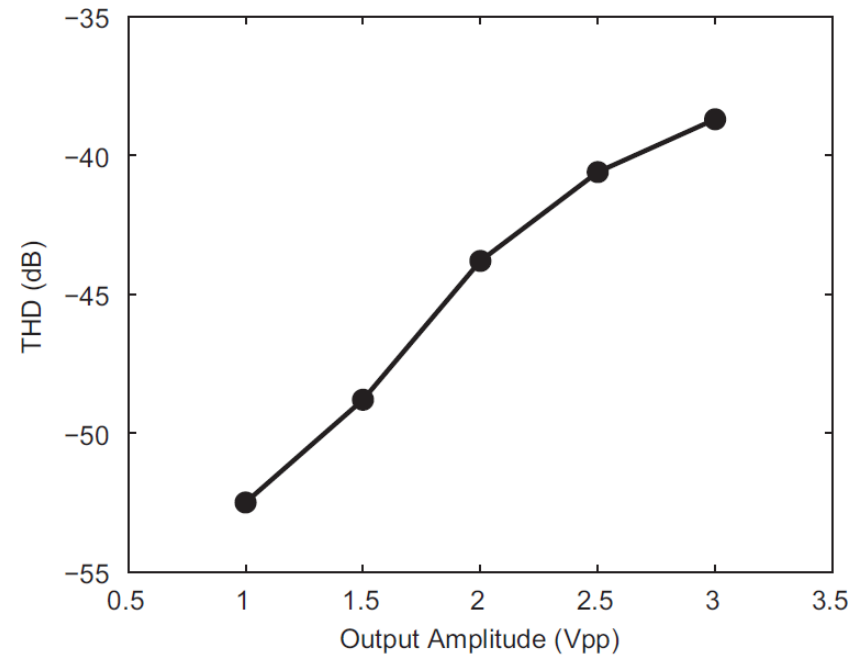

Measured harmonic distortion